

XIX

CSE251 - Mid Solve



VICTORUS AUT MORTIS

zqrif 31

MID Fall 24

1)

a) Assumption

- 1) Infinite open loop gain (A_{OL})
- 2) \parallel Input Resistance (R_{in})
- 3) Zero Output (R_{out})

b) $V_{out} = -\frac{1}{R_f C} \int V_{in} dt$

c) Non linear because, $I = I_s (e^{\frac{qV}{nkT}} - 1)$

d) Assumption of CVD Operating gate,

1) Forward biased (ON)

i) $I_D > 0$

ii) $V_D \approx 0.7$


2) Reverse Biased (OFF)

i) $V_D < 0.7$

ii) $I_D = 0$

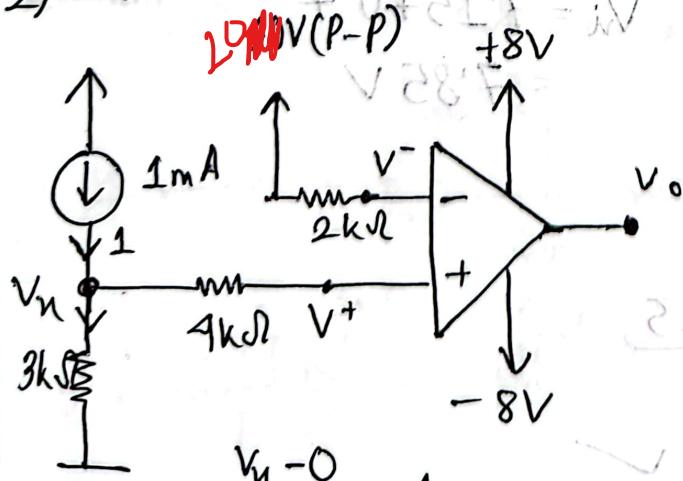
2) a)

It would be 10V (P-P) but as I have made the graph (mistakenly) I have assumed it was 20V (P-P)



$$\frac{V_o - 0}{3} = 1$$


$$\Rightarrow V_o = 3$$

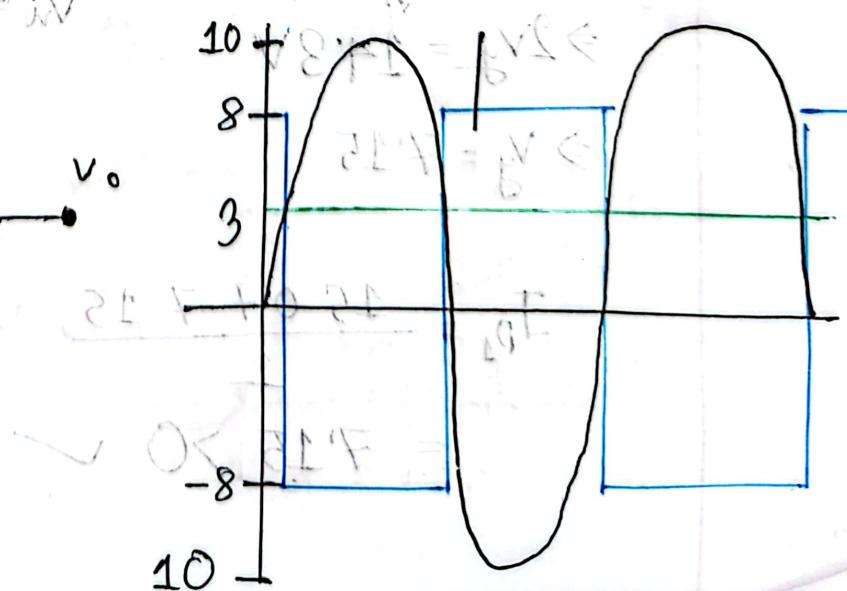

PQ Net DB

b)

Assuming D_1 ON, D_2 OFF

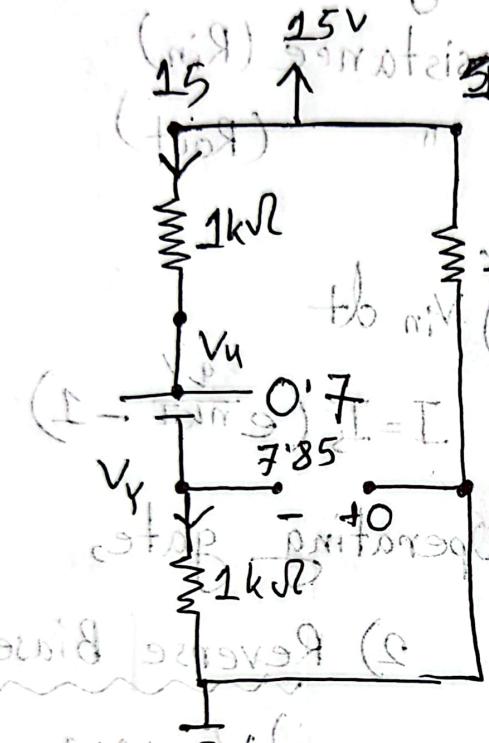

(No) So, D_2 is off ✓

Assumption right

Vy Node

$$\frac{15 - 0.7 - y}{1} = \frac{V_y - 0}{1}$$


$$\Rightarrow 2V_y = 14.3V$$

$$\Rightarrow V_y = 7.15$$

$$I_{D_1} = \frac{15 - 0.7 - 7.15}{1}$$


$$= 7.15 > 0 \quad \checkmark$$

$$V_x = 7.15 + 0.7 \\ = 7.85V$$

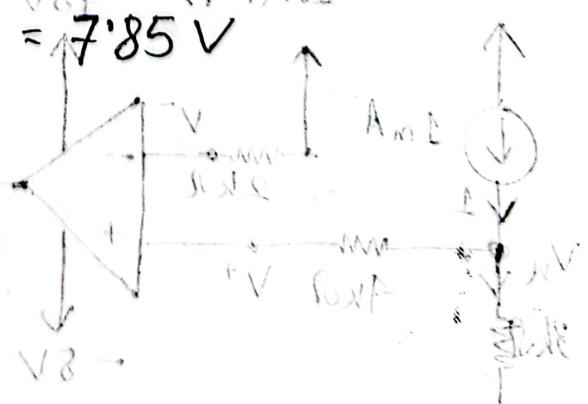

$$I = \frac{0 - N}{E}$$


$$E = N \in$$

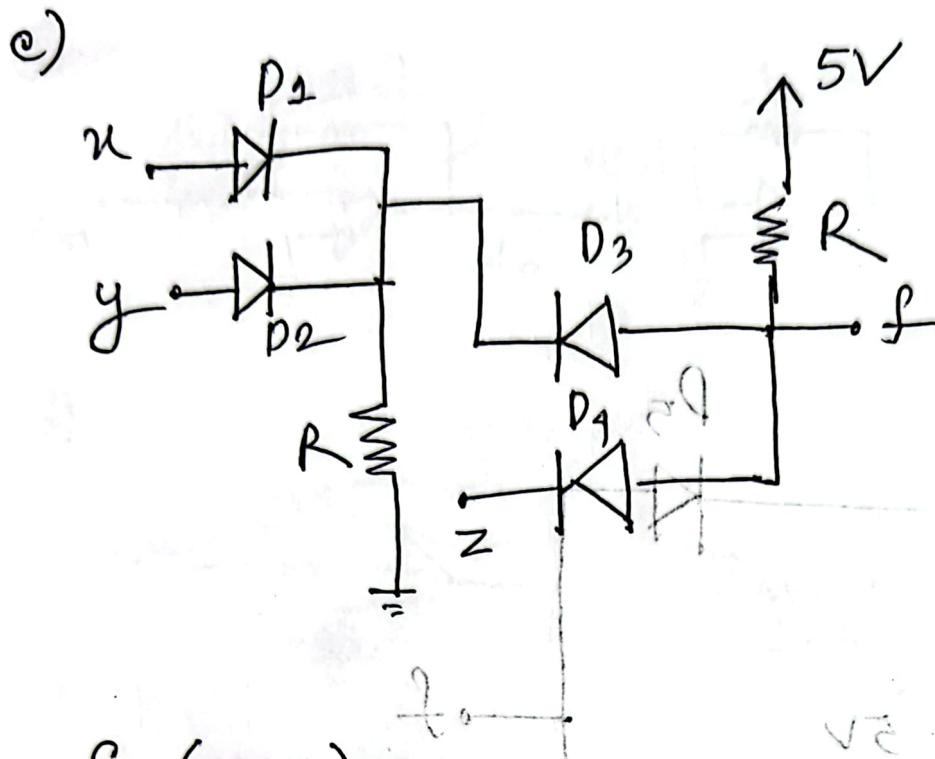

$$f = (x+y)z$$



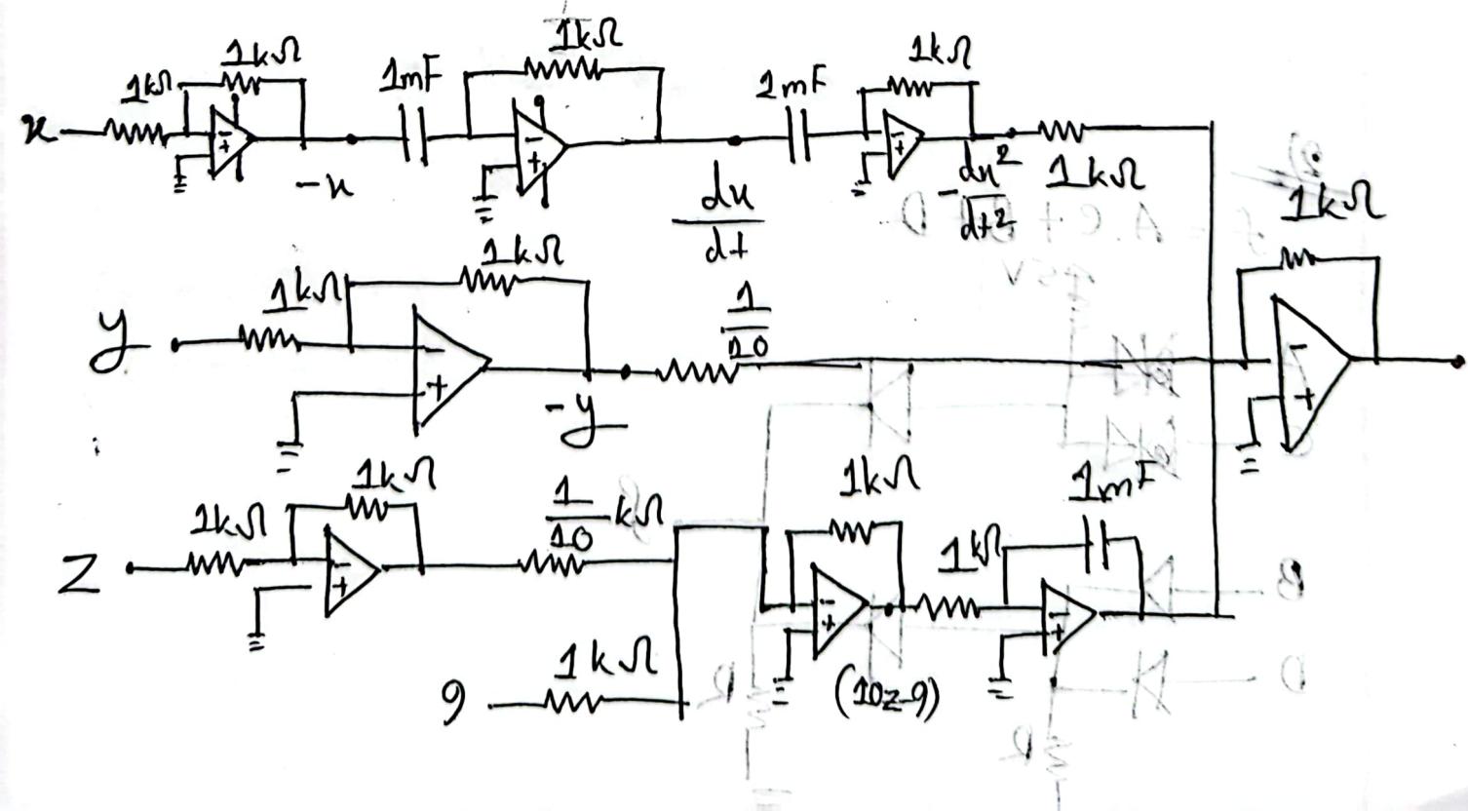
3) a)

$$\begin{aligned} f &= \frac{d^2u}{dt^2} + 10y + \int (10z - 9) dt \\ &= -\left(\frac{d^2u}{dt^2} - 10y - \int (10z - 9) dt \right) \end{aligned}$$



b)

$$f = A + C + B \cdot D$$

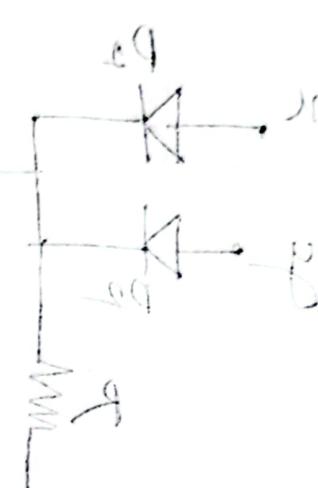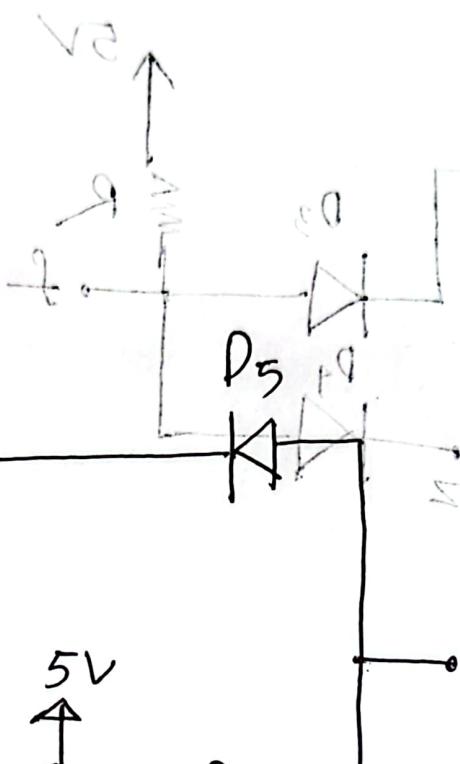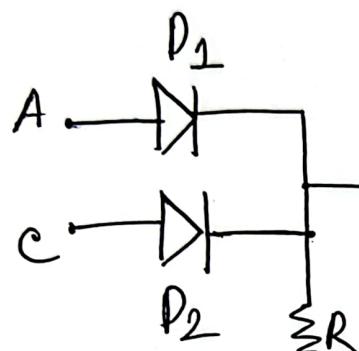


$$\Sigma(B+C) = 2$$

$$\frac{N^2b}{N+b} = 2$$

$$D \left(\frac{N^2b}{N+b} - \frac{N^2b}{N+b} \right) = 0$$


2)

$$f = A \cdot C + B + D$$

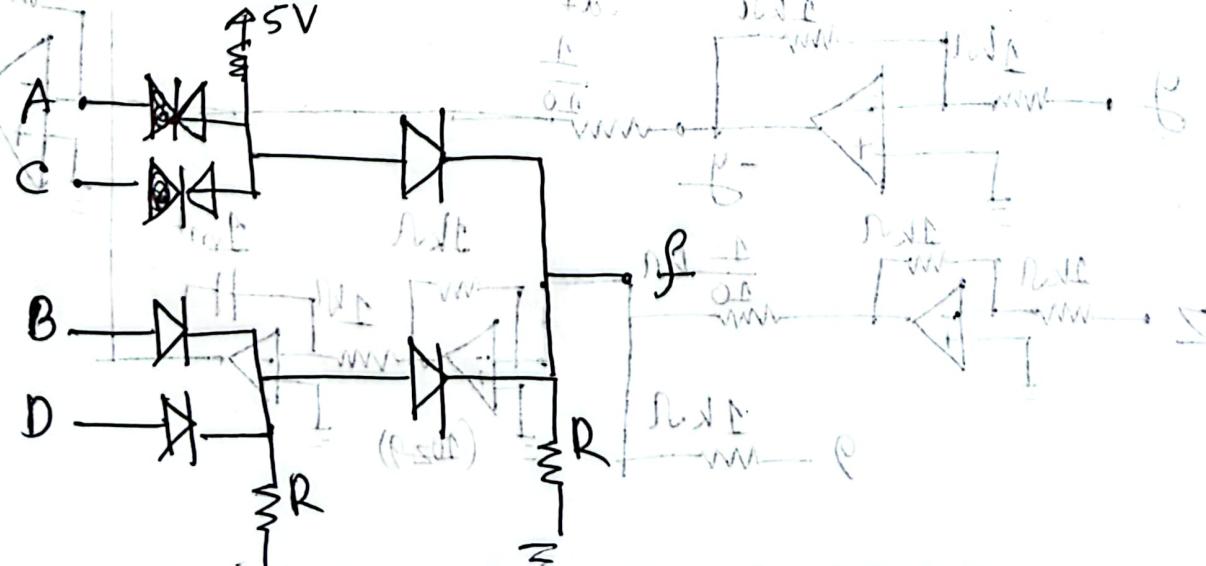


c)

c)

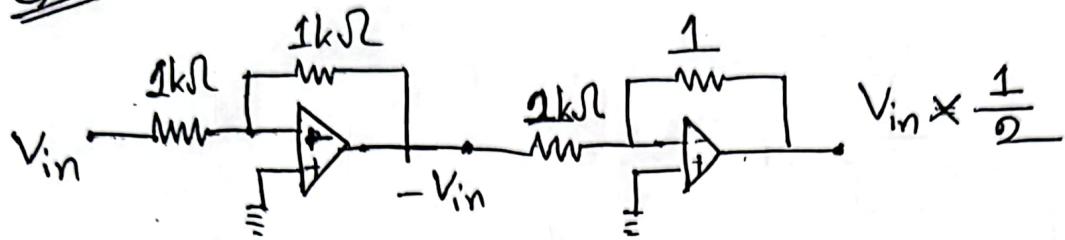

d)

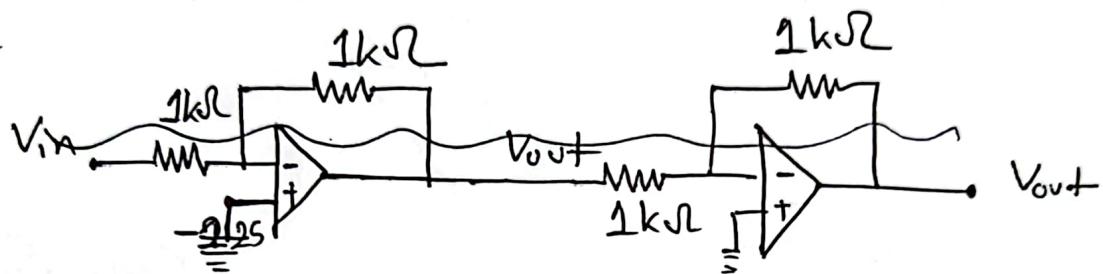


$$\frac{V_{in} - (-1.25)}{1} = \frac{-V_{out+} - 1.25}{1}$$

$$\Rightarrow V_{in} + 1.25 = -V_{out+}$$

$$\Rightarrow V_{out+} = -V_{in} - 2.5$$

After inverting,


$$V_{out+} = V_{in} + 2.5$$

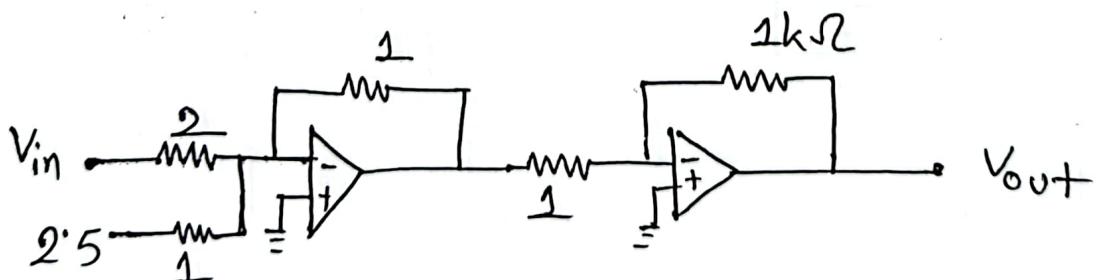

1)


- a) A virtual ground is a concept used in operational amplifier circuits, referring to a node or point in the circuit that is maintained at approximately zero volts (ground potential), despite not being physically connected to ground.

b)

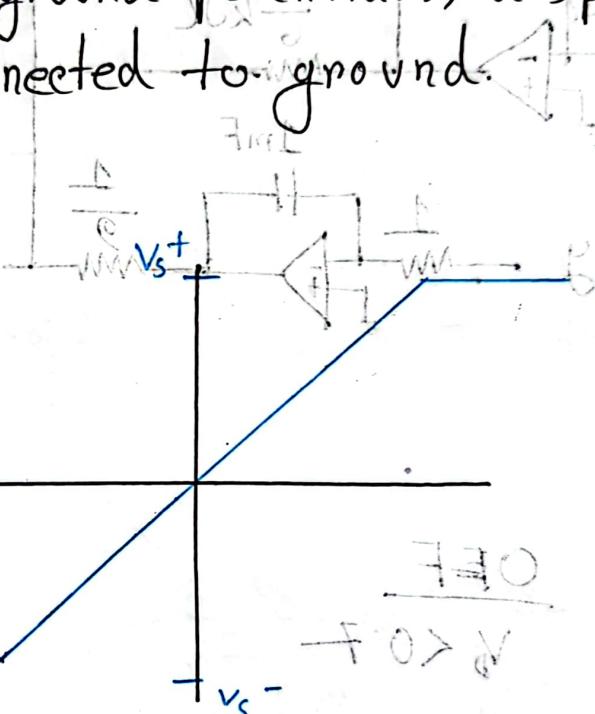

Non-inverting
amplifier
slope = 2

c)

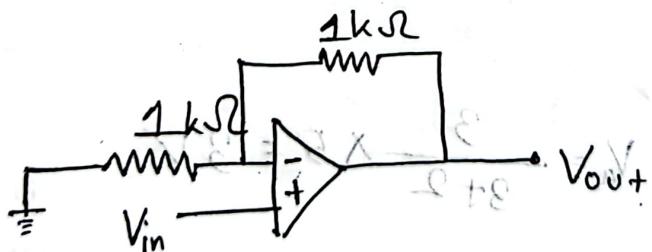

$$\left(1 + \frac{R_f}{R_i}\right) = 2$$


$$\Rightarrow R_f = R_i$$

d)

$$f = -3 \frac{dz}{dt} + 6u + 9 \int (y) dt$$

$$= -\left(3 \frac{dz}{dt} - 6u - 9 \int (y) dt\right)$$


PSOR 2019/2020 1.14

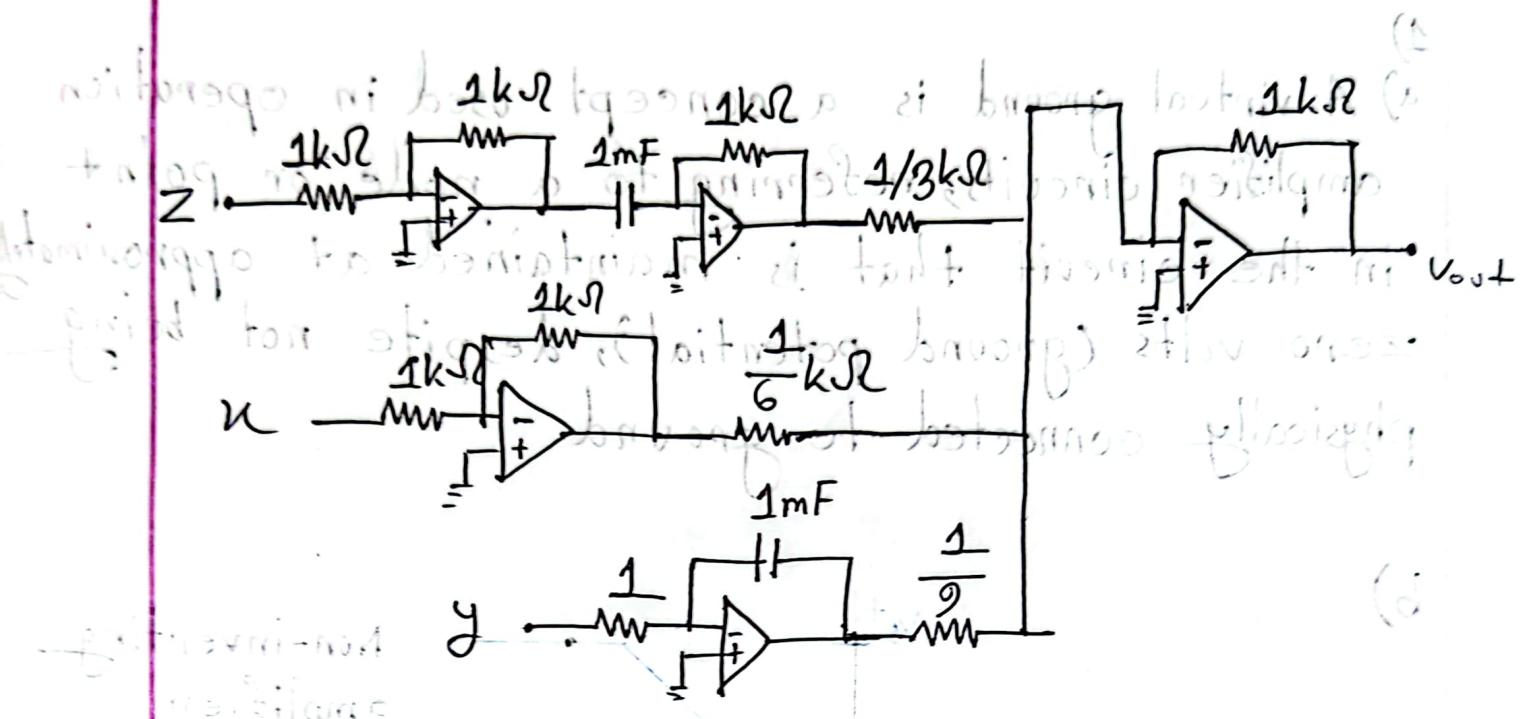


2)

a) ON
 $I_D > 0$

OFF
 $V_D < 0.7$

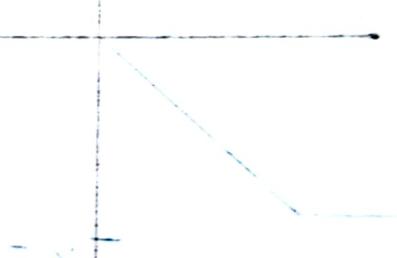

b)

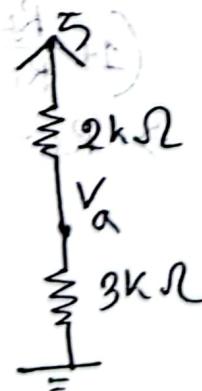


$$V_a = \frac{3}{3+2} \times 5 = 3 \text{ V}$$

$$\begin{aligned} & \text{For } V_b(+) : \frac{V_b - 0}{2} = 1 \\ & \Rightarrow V_b = 2 \text{ V} \end{aligned}$$

c)

Assuming D_1 ON, D_2 OFF

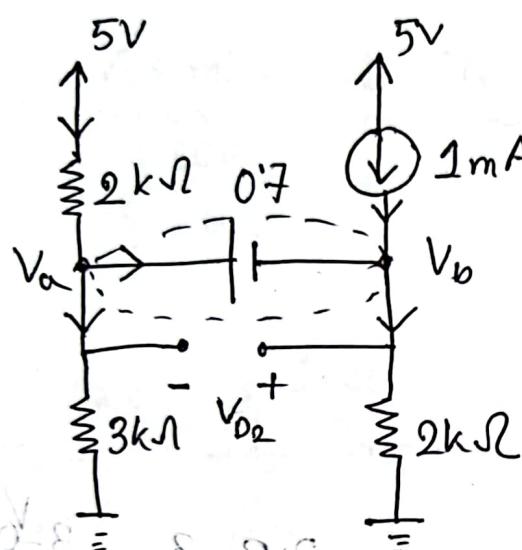

$$\frac{V_a - 0}{2k\Omega} = \frac{5 - V_a}{2k\Omega}$$

$$V_a = 2.89V$$

$$V_b = 2.187V$$

$$V_b < V_a,$$

$$\text{So, } I_{D1} = 0.092A > 0$$

d_2 in

reverse

bias

d) Both off, $I_{ab} = 0$

$$5V - \frac{2.89}{2} = 4.05V \quad (\sigma 8)$$

Supernode

$$\frac{5 - V_a}{2} + 1 = \frac{V_a - 0}{3} + \frac{V_b - 0}{2}$$

$$\Rightarrow 5 - V_a + 2 = \frac{2V_a}{3} + V_b$$


$$\Rightarrow 15 - 3V_a + 6 = 2V_a + 3V_b$$

$$5V_a + 3V_b = 21$$

$$V_a = V_b = 0.7$$


$$\frac{5 - V_a}{2} + \frac{0 - V_a}{3} = I_{D1}$$
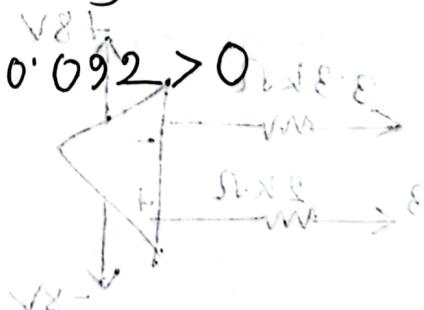
$$\Rightarrow \frac{5 - 2.89}{2} + \frac{-2.89}{3} = I_{D1}$$




$$3) a) V_{out} = -\frac{R_f}{R_i} V_{in}$$

b)

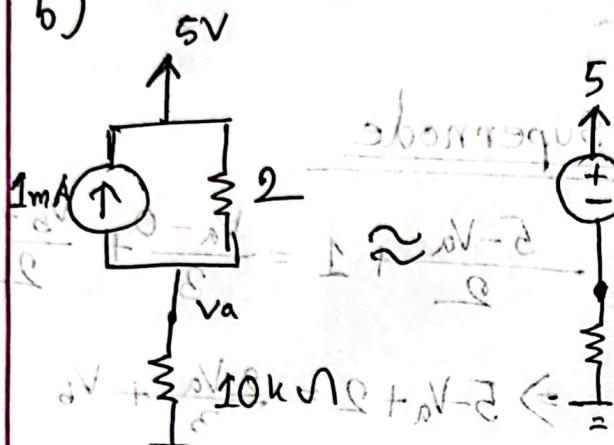


$$\therefore V_a = V_+ = 5 - \frac{2}{2+10} \cdot 10 = 3V$$

FET on drain

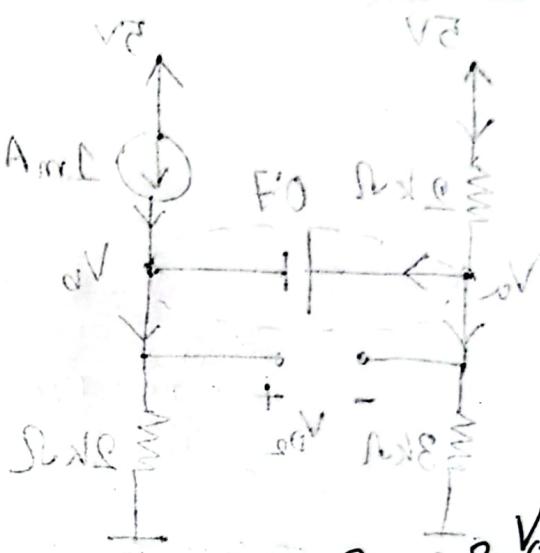


$$\frac{3 \cdot 3 - 3}{10} = \frac{0.3}{0.33}$$

$$\Rightarrow V_o = 2.97525V$$

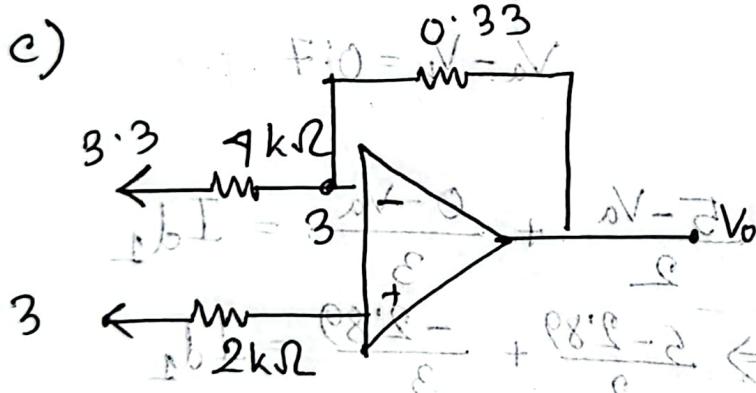



$$0.33 > 0.2$$

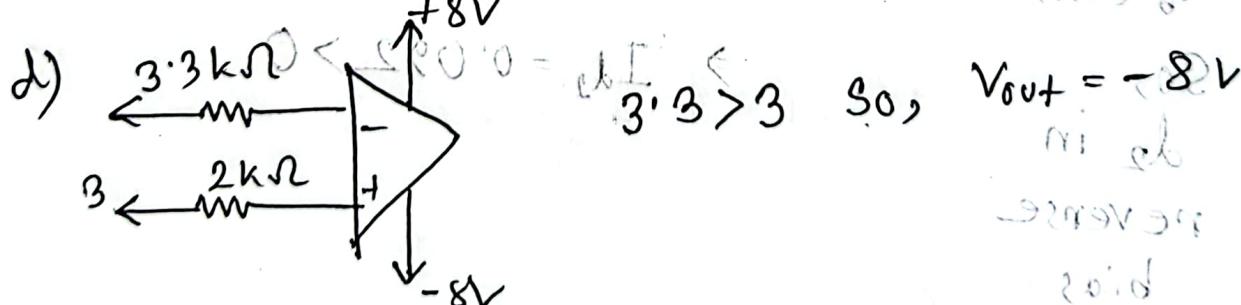


$$0.33 < 0.2$$

e)

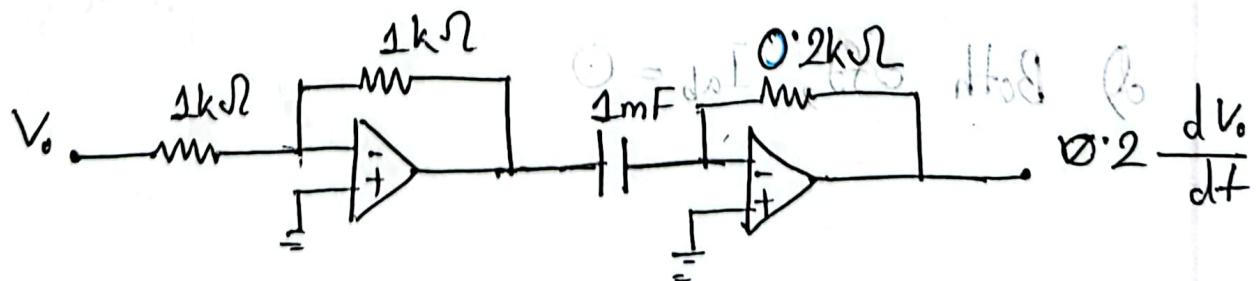

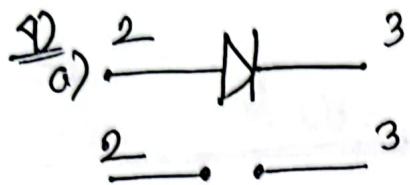

b) Assuming D_2 ON, D_1 OFF

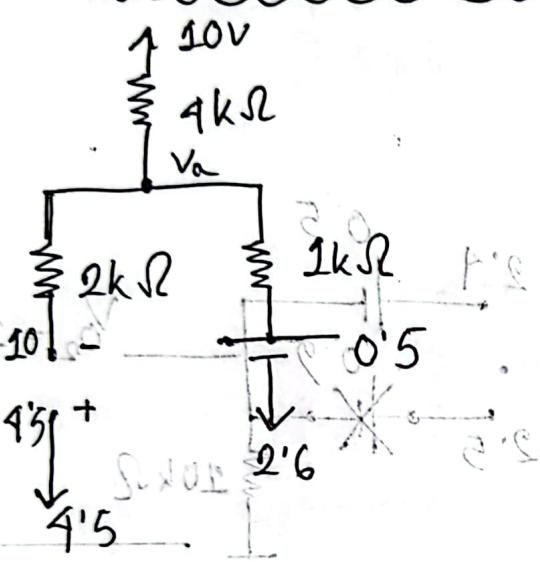

$$I_{D2} = \frac{10 - 3.1}{1} = 1.38 \text{ mA} > 0$$

$10 > 9.5$, D_1 in reverse Bias

$$I_{D1} = 0$$

$$\frac{10 - V_a}{4} = \frac{V_a - 3.1}{1}$$

$$\Rightarrow 10 - V_a = 4V_a - 12.4$$

$$\Rightarrow 5V_a = 10 + 12.4$$


$$\Rightarrow V_a = 4.48 \text{ V}$$

Non inverting

$$V_o = \left(1 + \frac{R_f}{R_i}\right) \times V_{in}$$

$$= \left(1 + \frac{1}{1}\right) \times 4.48$$

$$= 9.6 \text{ V}$$

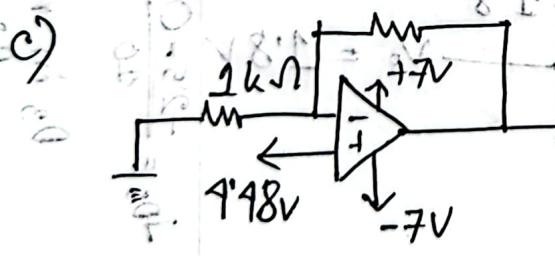


NO D_3 \Rightarrow $V_o = V_{in}$



$V_o = V_{in}$

5)

a)

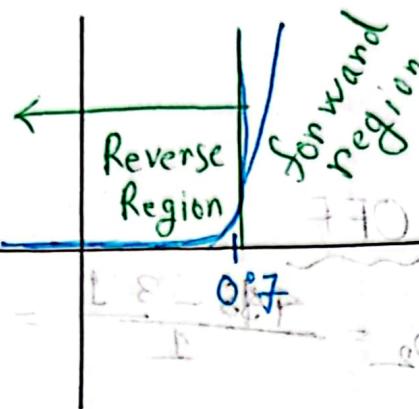



$$0 < A_{m3} \cdot D =$$

$$0.7$$





(d) ON D₃ OFF D₁ - Inverted



b)

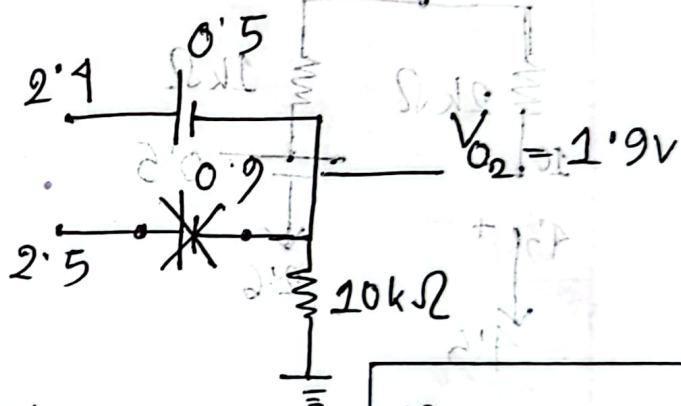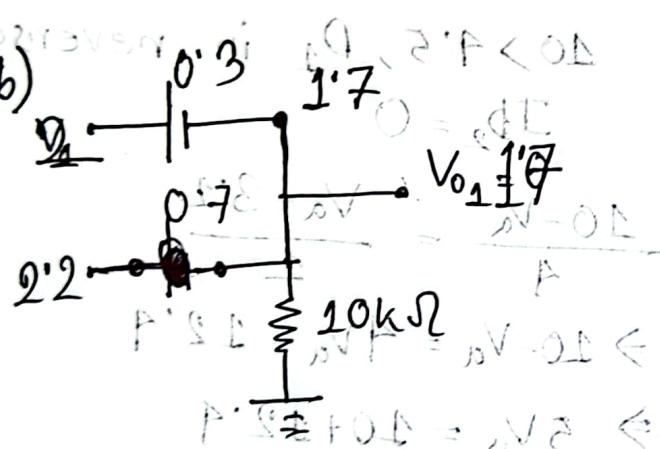


c)

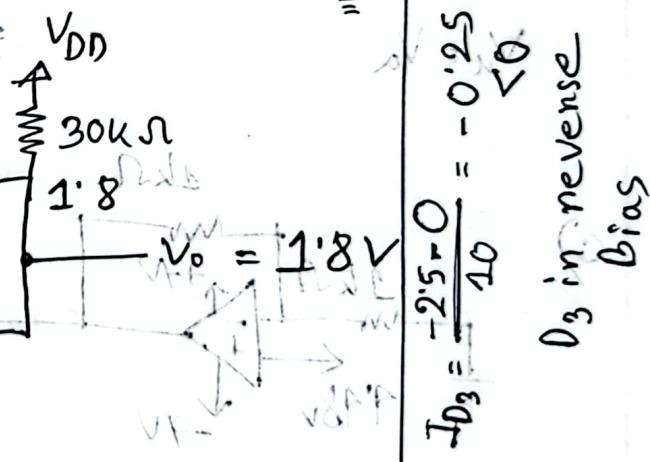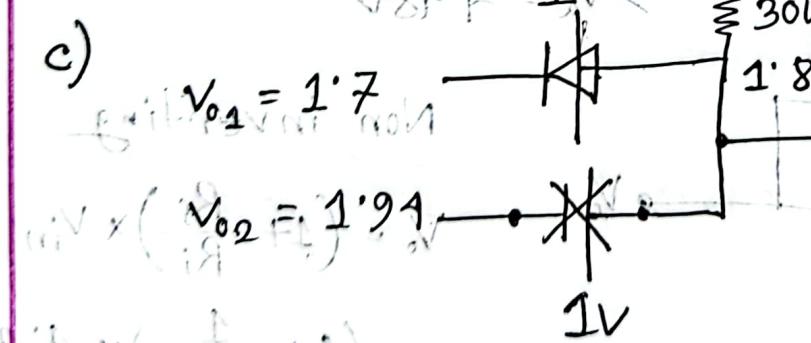

d)

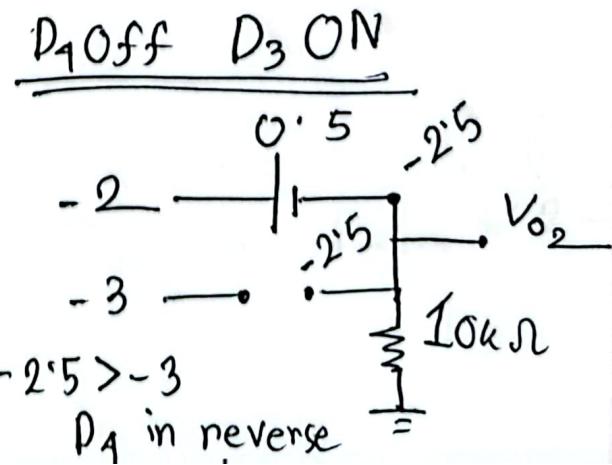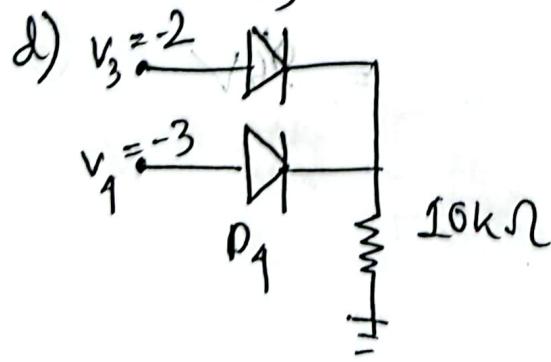


S_0 ,
 D_1 off D_2 off

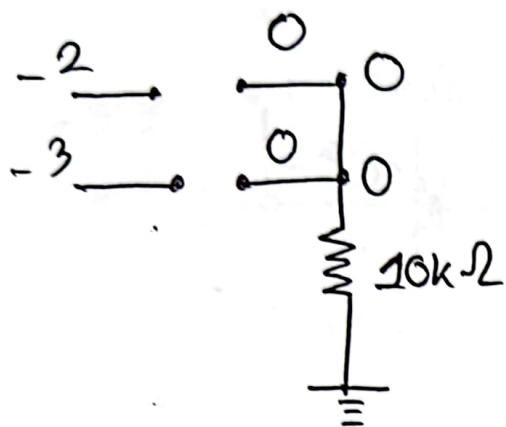

$$0 > -2 > -3$$

S_0 , both in reverse


$$I_{D1} = I_{D2} = 0$$

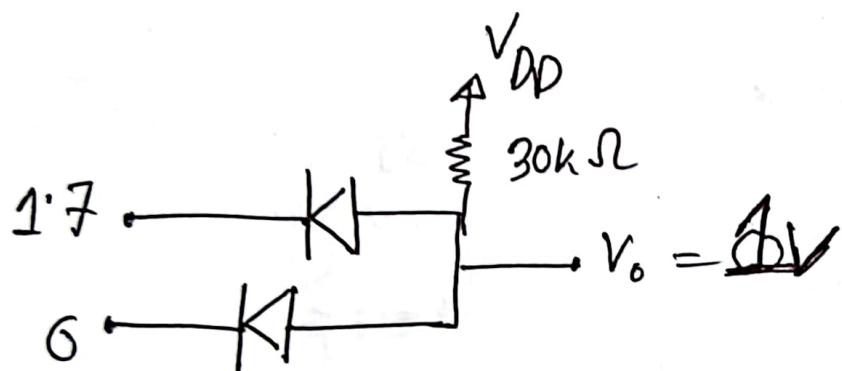

Mid Spring

Summer 21

1) a) AND Gate

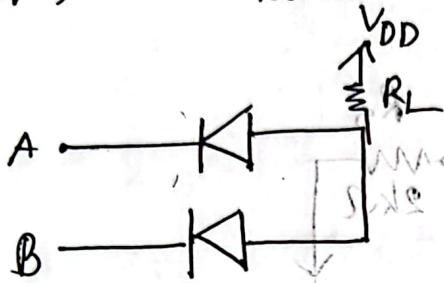


$$V_A = 4V \quad V_B = 5V \quad (a)$$

$$V_B = 5V$$

$$V_A < V_B \quad \text{So, } f = V_A$$

c)

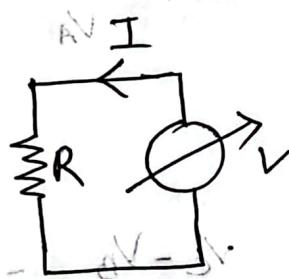

$$\text{slope} = \frac{y_2 - y_1}{x_2 - x_1} = \frac{0.5 - 0}{1 - 0} = 0.5$$

$$R = 2$$

$$\frac{0.5 - 0}{2} = \frac{0.5 - 0}{0.5}$$

$$V_D - D_2 = V_D - V_D \in$$

Assuming D_2 ON, D_1 OFF

$$V_D - D_2 = V_D - V_D \in$$

$$2.5 = V_D - 5 \in$$

$$2.5 = \frac{1}{2} \times 5 \in$$

$$2.5 = 2.5 \in$$

$$5 > 1$$


So, D_1 is in

reverse
Bias

$$I_{D_1} = 0$$

$$\frac{V_D - 0}{2} = \frac{5 - 0}{2}$$

$$V_D = 5V \in$$

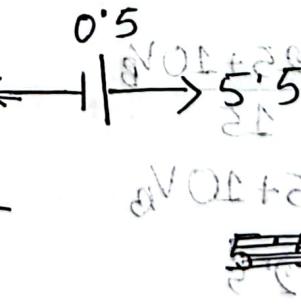


$$V_{D2} = V_D + 2.5 \in$$

$$V_{D2} = 0 \in$$

$$I_{D_2} = \frac{5 - 0}{2} \\ = 2.5A > 0$$



$$V_D = 5V \quad 0.5 < 0V \quad (b)$$

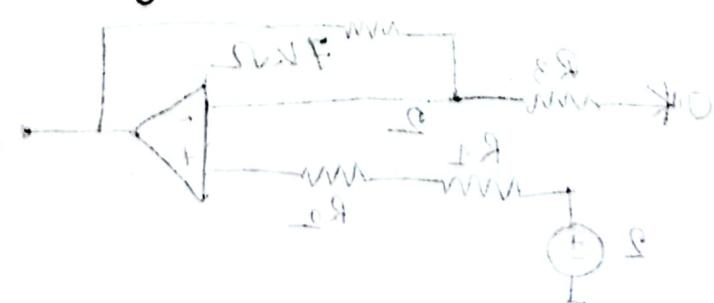

- bringt hilf
zu ermitteln

3)a) $I^- = I^+ = 0$ (d)

b)

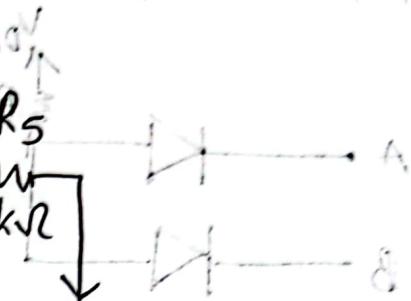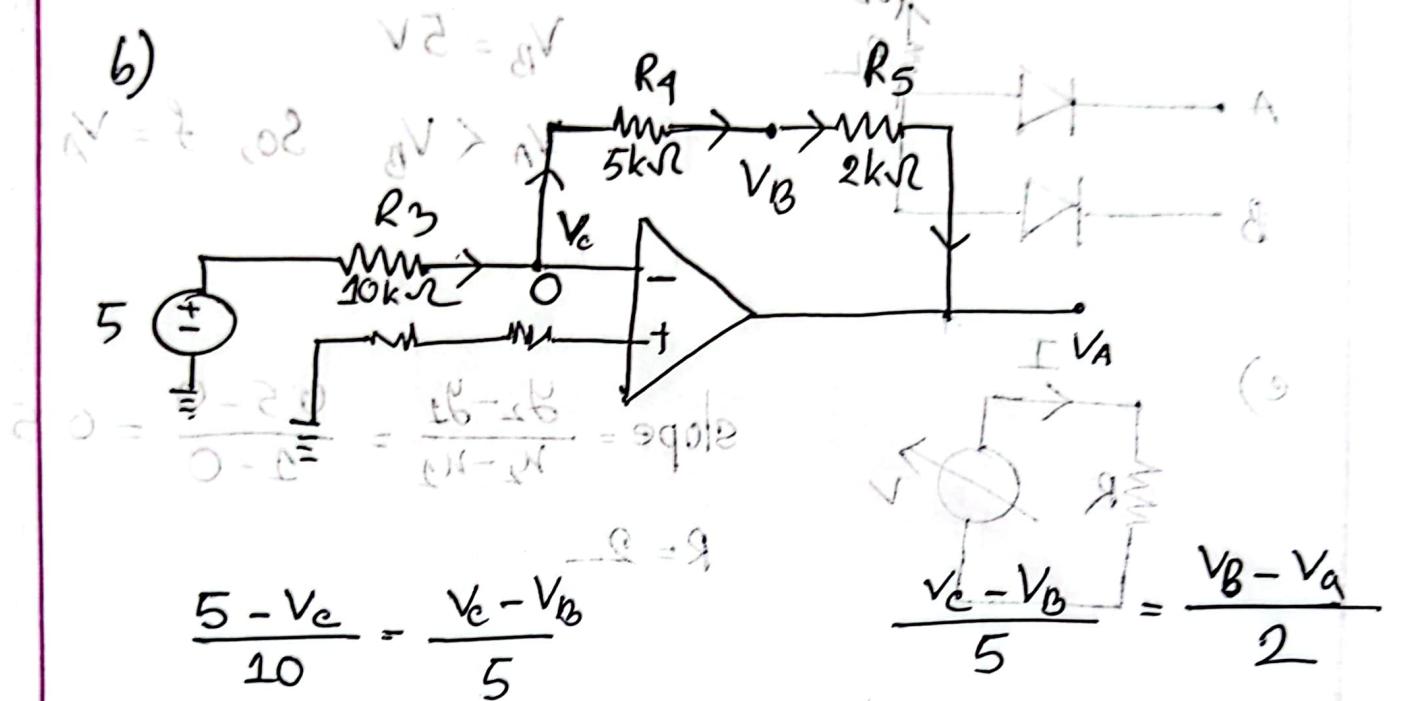

$$\frac{V_c - V_B}{5} = \frac{V_B - V_A}{2}$$

$$\Rightarrow 2V_c - 2V_B = 5V_B - 5V_A$$


$$\Rightarrow -2 \cdot (-2.5) = 5 \cdot (-2.5) = -5V_A$$

$$\Rightarrow 5 + 12.5 = -5V_A$$

$$\Rightarrow V_A = -3.5$$

c) $V_B > V_A$ So, $V_{sat} = 5V$

d)

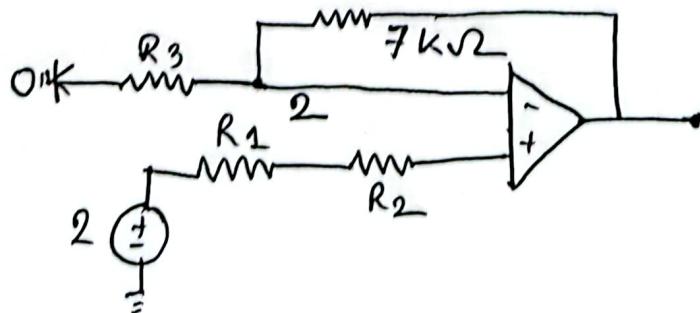

$$O = \frac{V_A - V_B}{R_3} = \frac{2 - 5 \cdot 13}{7}$$

$$5 \cdot 13 = 65 \Rightarrow R_3 = 4.77$$

$$\textcircled{e} \quad \frac{2 - V_B}{5} = \frac{V_B - 5.13}{2}$$

$$\Rightarrow 7V_B = 29.65$$

$$\Rightarrow V_B = 4.24$$

A)

a) $V_s(G) = 6G^2 + 7G$


$\underline{V_s(16)} = 6 \times (16)^2$

$$V_s(0.186) = 6 \times (0.186)^2 + 7 \times 0.186 \\ = 1.51 \text{ V}$$

b) Before 16:00 $V_s > 1.51$

After 16:00 $V_s < 1.51$

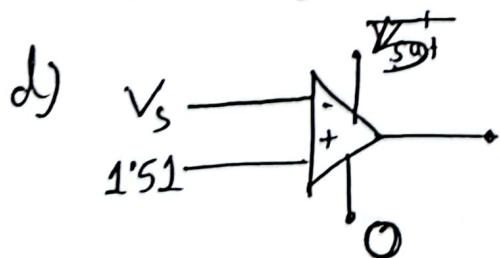c) Inverting comparator to satisfy "lamp on at lower V_s "



e)



$$V_o = X_1 V_1 - X_2 \int V_2 dt$$

$$= 3V_1 - 10 \int V_2 dt$$



$$= -(-3V_1 + 10 \int V_2 dt)$$

$$X_1 = 1+2 = 3$$

$$X_2 = 1+9 = 16$$

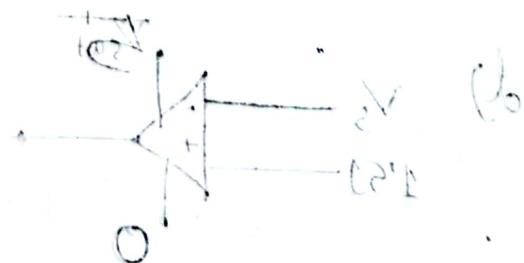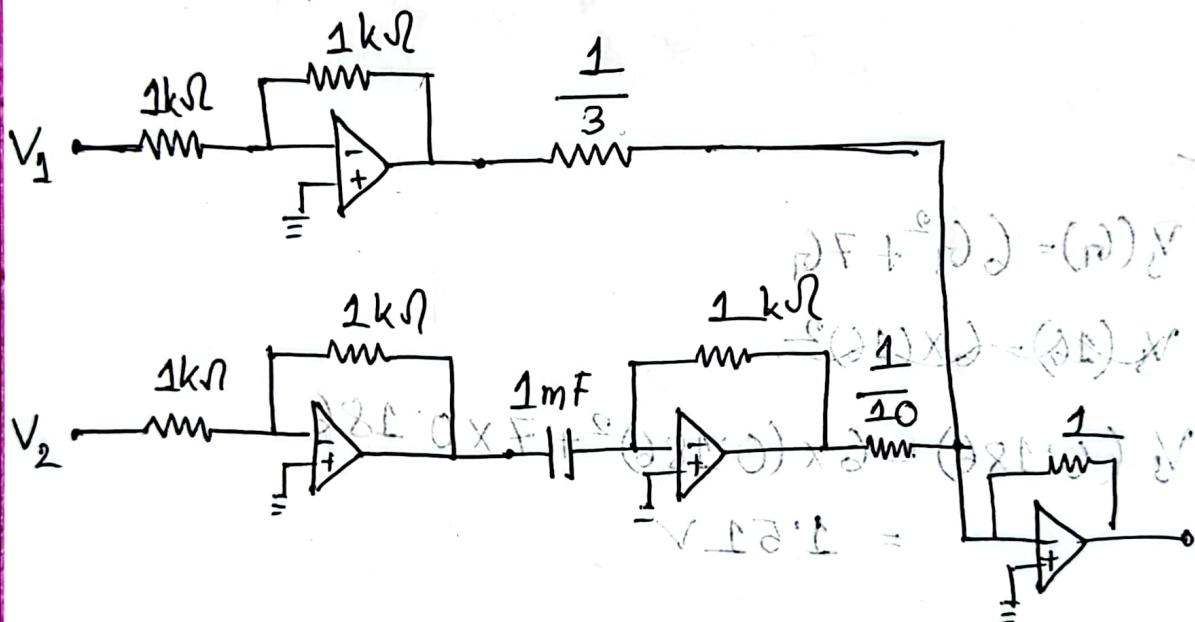

Summer 23

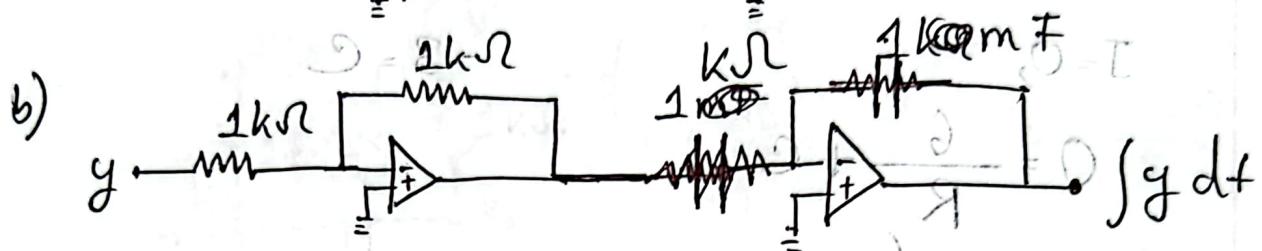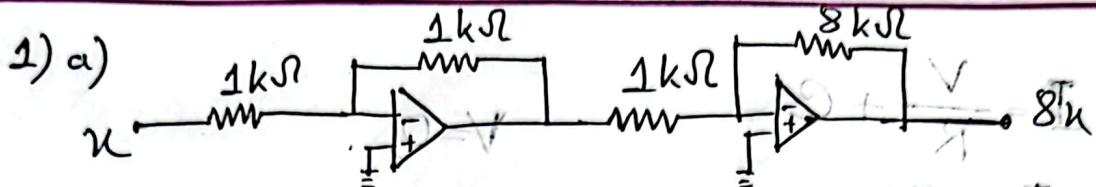


c)

$$f = -4u - \int y dt + 2 \frac{dz}{dt} = -\frac{d}{dt} \left(2z \right) = 8 \left(\frac{d}{dt} z \right)$$

d)
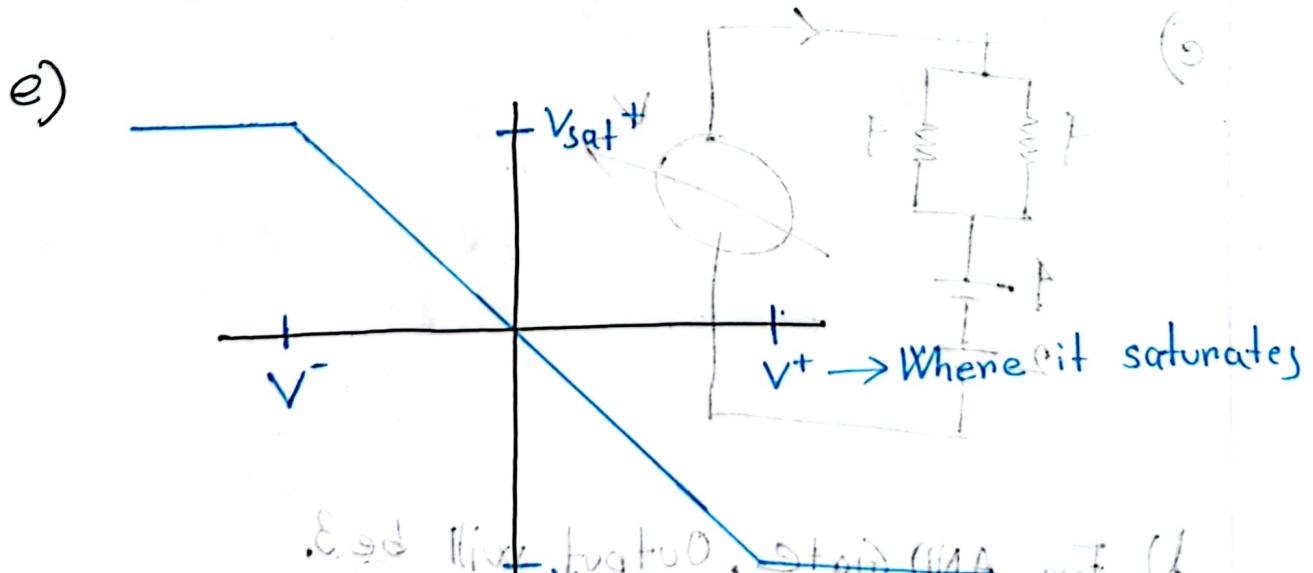
$$\begin{aligned} f &= -4x_1 - \int 8 \cos(30t) dt + 2 \times \frac{d(\sin(4t))}{dt} \\ &= -4 - \frac{8 \sin(30t)}{30} + 2 \times \frac{4 \cos(4t)}{4} \\ &= -4 - \frac{1}{15} \sin(30t) + 8 \cos(4t) \end{aligned}$$




End line bug to 0, start GAA not 0
start not bug

$\mathcal{E} \Omega$ 93mm2

3)a)

$$I = \frac{V}{R} + C$$

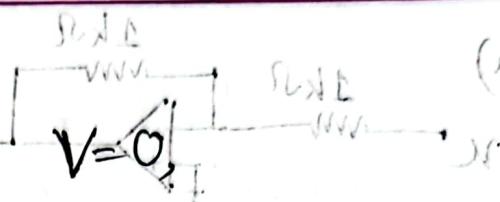

(a)



$$I = 0$$

$$Q = \frac{6}{R} + C$$

$$\Rightarrow -C = \frac{6}{R}$$

$$\Rightarrow R = \frac{6}{-C} = \frac{6}{\frac{6}{100}} = 100 \Omega$$

b)

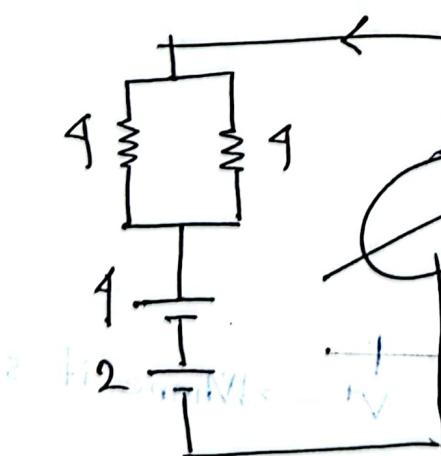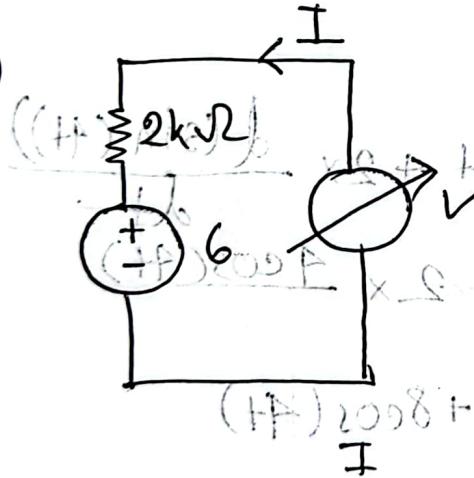

c)


(b)

d) For AND Gate, Output will be 3.

And for OR Gate, " " " 5.

1)

a) Assuming D1 ON

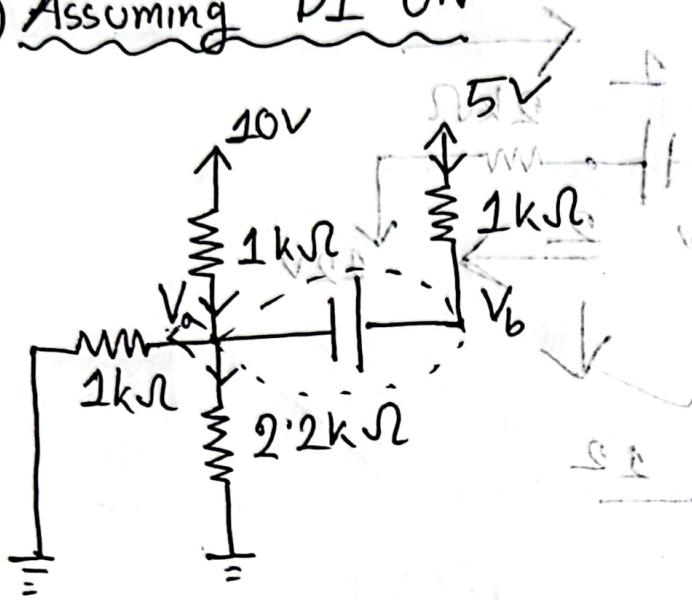

$$V_b - V_a = 0.7$$

$$\frac{10 - V_a}{1} + \frac{5 - V_b}{1} = \frac{V_a - 0}{2 \cdot 2} + \frac{V_a - 0}{1}$$

$$\Rightarrow 10 - V_a + 5 - V_b = 0.45 V_a + V_a$$

$$\Rightarrow 15 - 4.45 V_a = 15$$

$$\Rightarrow V_a = 4.35$$

~~$$10 - V_a + 5 - V_b = 0.45 V_a + V_a$$~~

$$\Rightarrow 15 = 2.45 V_a + V_b$$

$$V_a = 4.19 V$$

$$V_b = 4.84 V \text{ (Ans.)}$$

$$I_{D1} = \frac{4.19 - 16}{1} + \frac{4.19}{1} + \frac{4.19}{2 \cdot 2}$$

$$= 0.162 > 0$$


Assumption right

~~b) i) $V_+ = 4.84 V$~~


~~ii) $V_- = 4.84 V$~~

$$c) V_r = \left(1 + \frac{1.8}{1.2}\right) \times 4.84$$

$$= 12.1 V$$

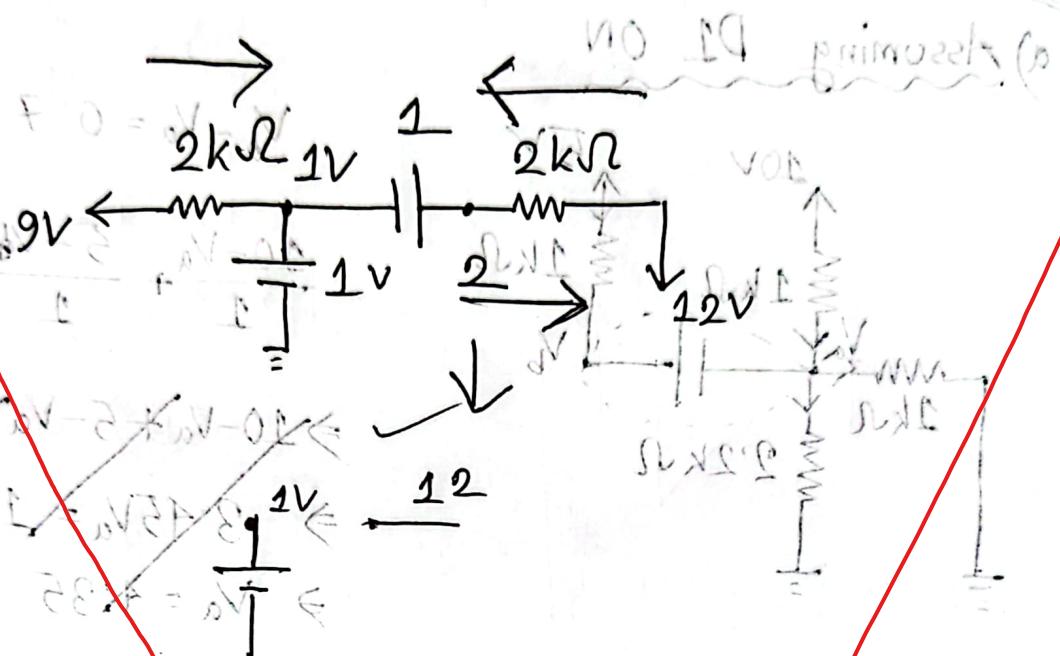
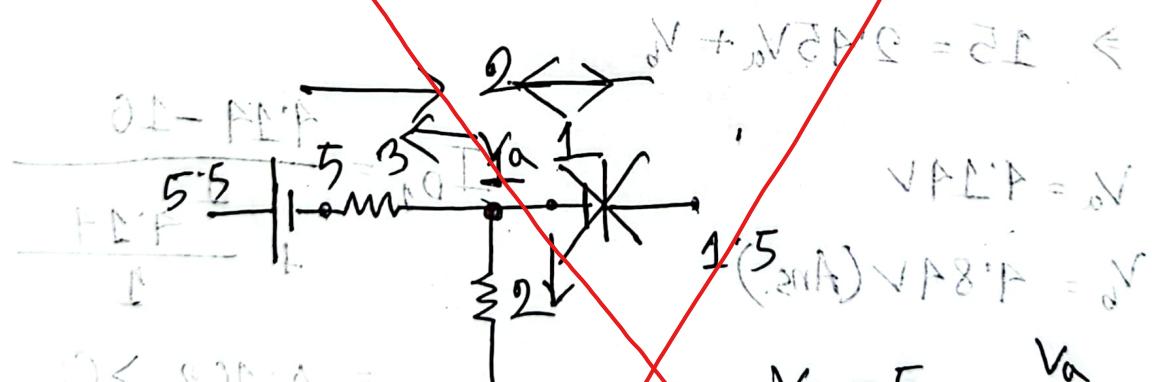
$$10V + \frac{9-1}{2} + \frac{12-1}{2} = 9.5$$



$$I = \frac{V_a - 5}{3} + \frac{V_a}{2}$$

$$\sqrt{V^2 + I^2} = \frac{2(V_a - 5) + 3V_a}{6}$$

$$\sqrt{V^2 + I^2} = \frac{2(1-5) + 3 \times 1}{6}$$


$$P_{G.P} \times \left(\frac{8.5}{8.5 + 1} + 1 \right) = V \quad (b)$$

$$\sqrt{V^2 + I^2} =$$


Spring 2023

1)

a)

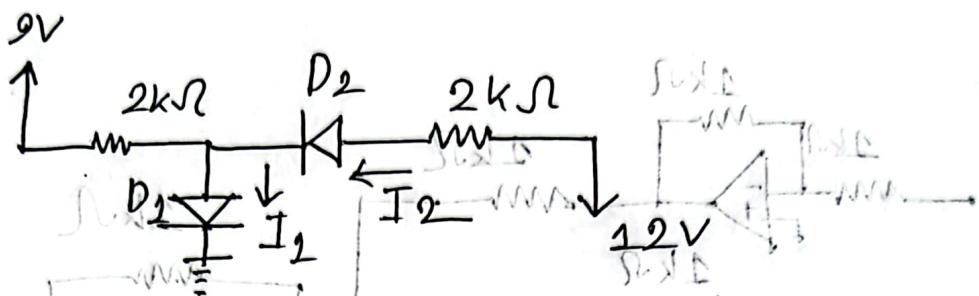

b) Assuming D_1, D_2 ON

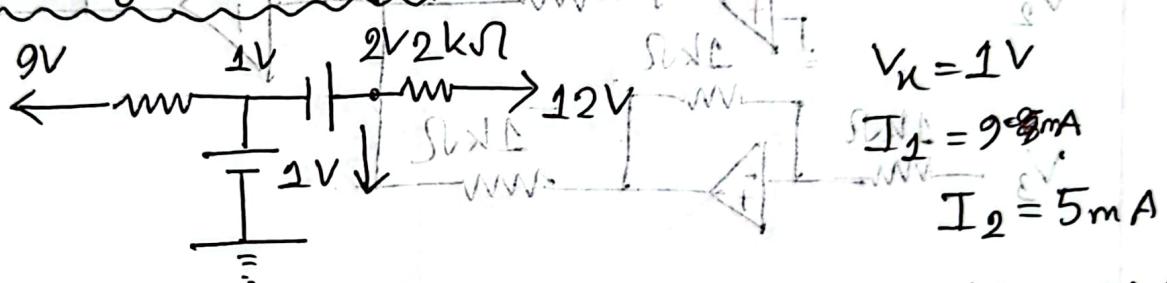

$$I_{D1} = \frac{9-1}{2} + \frac{12-1}{2} = 9 > 0 \quad V_y = 2V$$

Assumption right

$$\mathcal{E} = 1V$$

c) $P_{D1} = V \times I = 1 \times 9 = 9 \text{ watts}$ (Consuming)

2) a) $I = \frac{V}{R} + C$

$$I = 0,$$

$$R = \frac{5}{-C}$$

$$= 5k\Omega$$

$$x = 5V$$

$$y = 5k\Omega$$

x Voltage source


y resistor

c) Thienvin

ES02 gründ

3)

a)

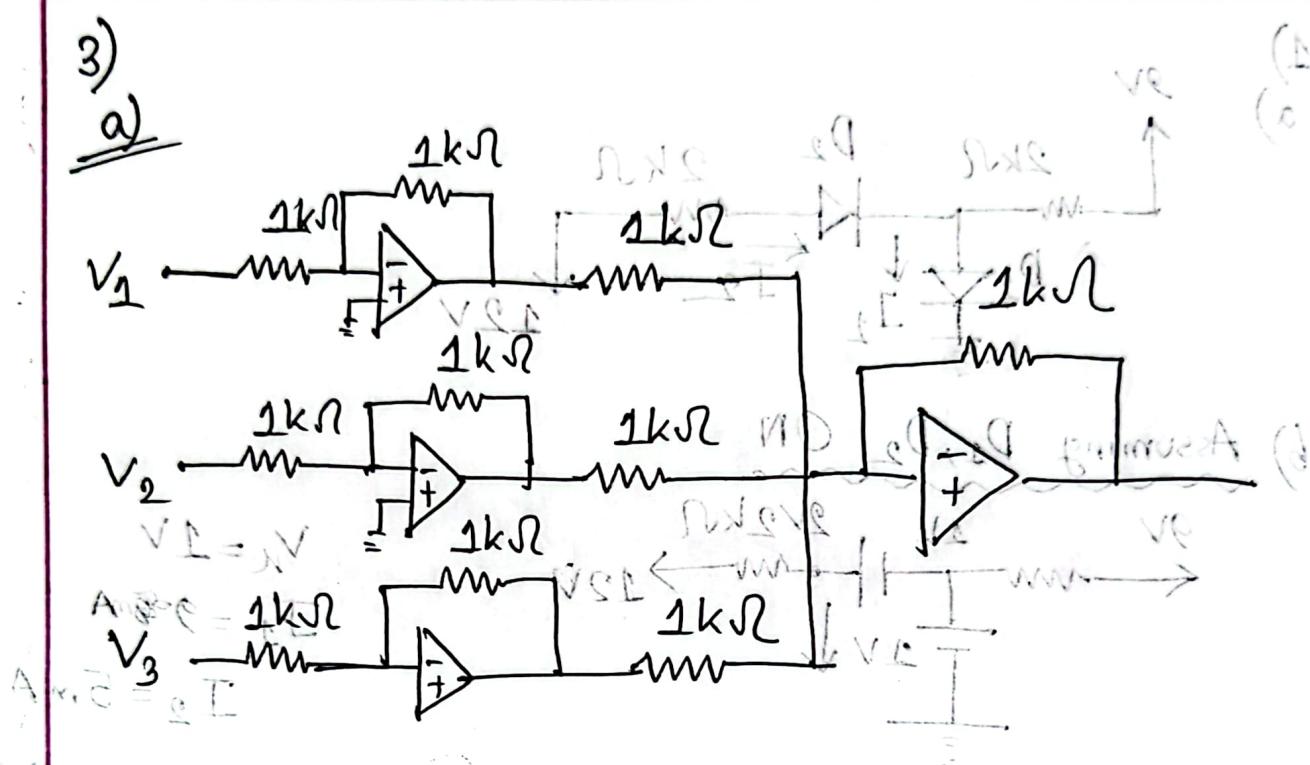


b) 6V

$$15 \times \frac{1}{k} = 5 + \frac{1}{k} \Rightarrow k = 3$$

Hilfe nicht mehr A

c)

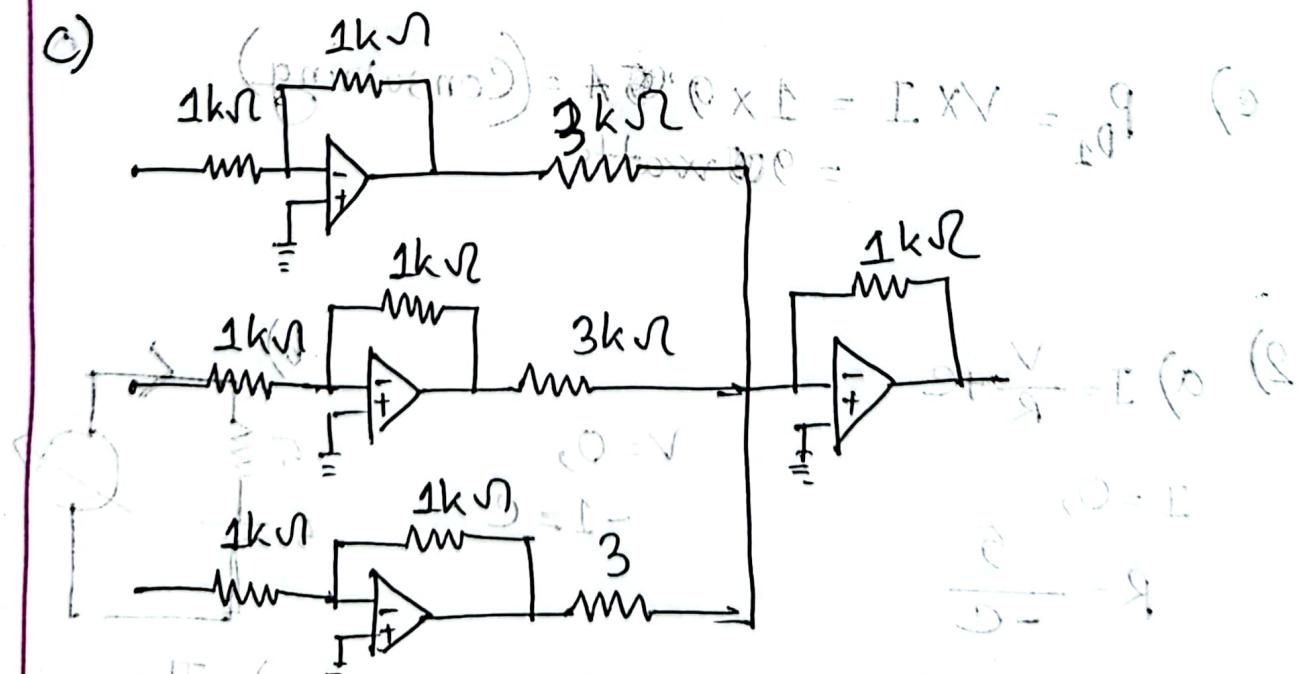

ausser (3) = 2000000000V X

richtig Y

15V =

$\sqrt{3} = 3$


$\ln(2) = 1$

$$d) \frac{V_{in} - 2.5}{3} = \frac{2.5 - V_{out}}{5}$$

$$V_{in} = \frac{19.5 - 3V_o}{5}$$

$$V_{TQ} = \frac{19.5 - 0}{5} = 3.9V$$
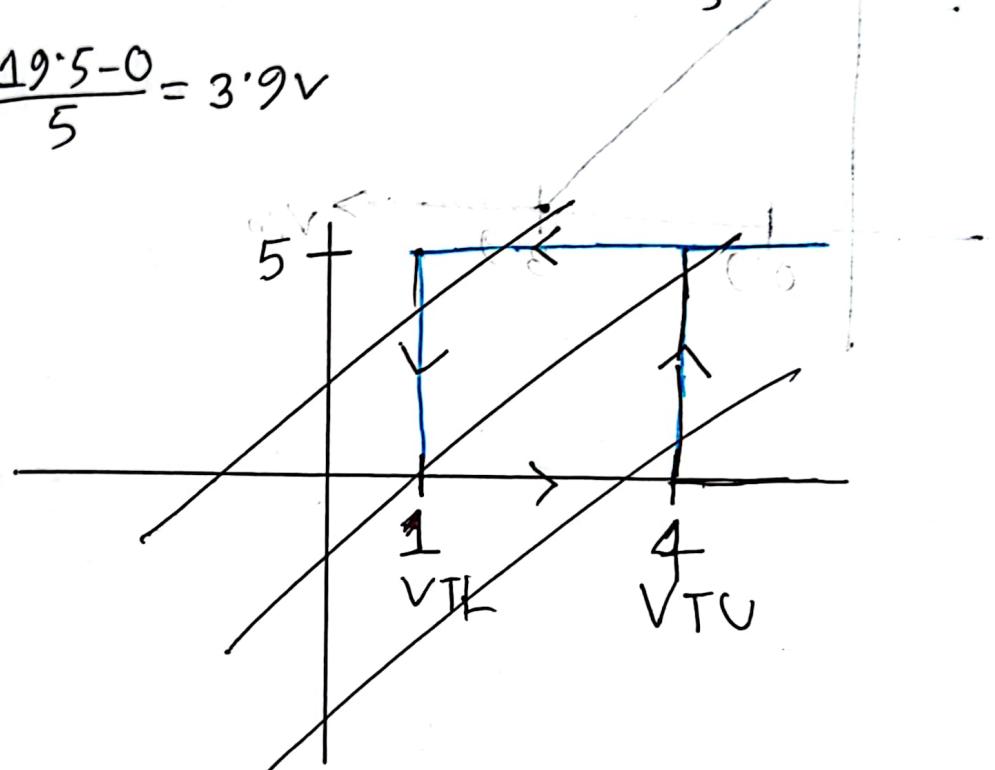
$$V_{TL} = \frac{19.5 - 3 \times 5}{5} = 0.9V$$




$$4) a) f = (a, b) + c$$


$$b) V_y = \left(1 + \frac{20}{5}\right) \times 2 \sin t \\ = 10 \sin t$$

$$b) V_i = 1 - 0.5 \cos t$$

$$V_o = 2 \sin t$$

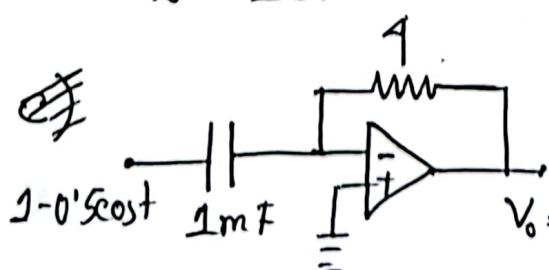
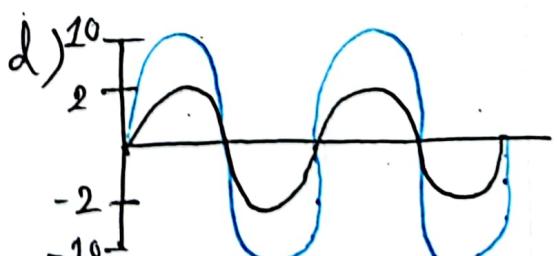
$$V_o = -4 \frac{d(1 - 0.5 \cos t)}{dt} \\ = 2 \sin t$$




~~$$V_o = \left(-\frac{5}{3}\right) V_{in} + \frac{19.5}{3}$$~~

$$\frac{V_o - V_{in}}{2} = \frac{2.5 - V_{in}}{3}$$

$$\frac{V_o - 3.0}{2} = V$$

$$V_o = \frac{0 - 3.0}{2} = 1.5V$$

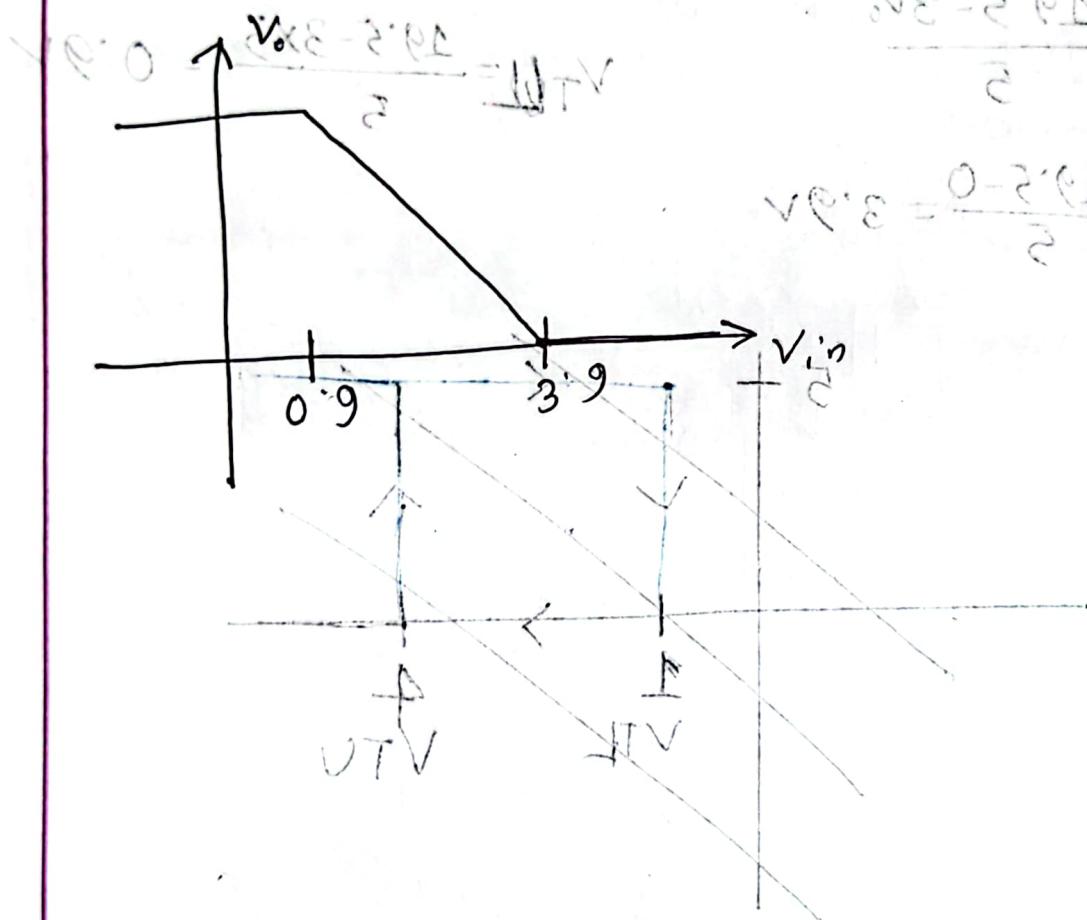


$$+2.5 \times \left(\frac{0.2}{2} + 1\right) = 1.5$$

$$5 + (1, 0) = 2$$

$$+2.5 \times 0.2 = 0.5$$


$$+2.5 \times 0.2 = 0.5$$

$$1.5 + 0.5 = 2$$

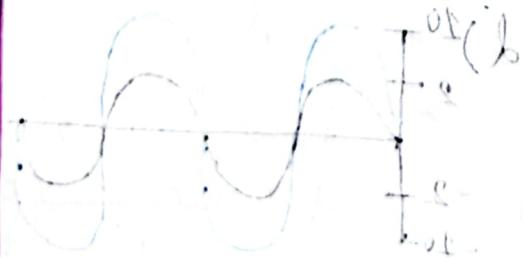


$$+2.5 \times 0.2 = 0.5$$

$$1.5 + 0.5 = 2$$

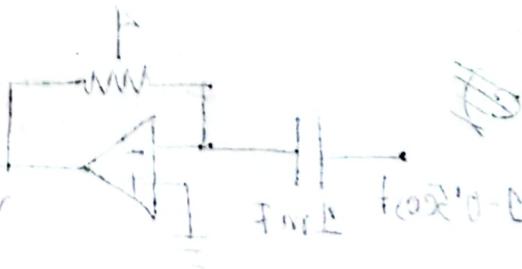

Summer-22

a) $V = -1$

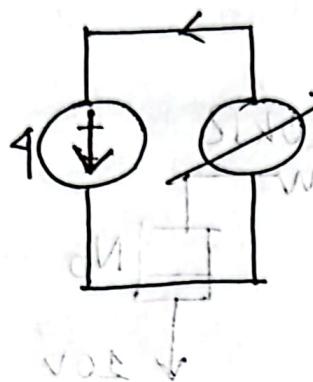

$$m = \frac{y_2 - y_1}{x_2 + x_1}$$

$$= \frac{1+1}{2+2} = 2$$

$$R = 3.3$$

$$I = \frac{V}{R} + C$$

$$\Rightarrow 1 = \frac{2}{3.3} + C$$

$$\Rightarrow C = 3.4$$

$$V = 0,$$

$$I = 3.4$$


$$I = 0,$$

$$\text{Ansatz } V_I = \frac{1}{3.3} R - CR = -3.4 \times 3.3$$

$$\text{Ansatz } I = \frac{1}{3.3} R$$



$$\text{Ansatz } I = \frac{1}{3.3} R$$

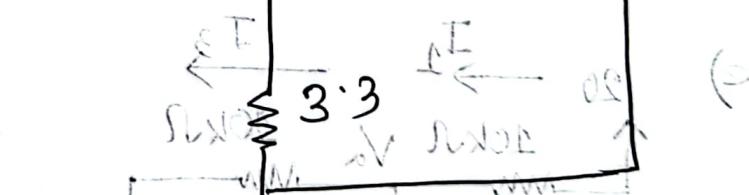

$$-CR = -3.4 \times 3.3$$

$$= -11.22$$


b) CD. $I = \frac{3}{880 - 3.3} + 3.4 = 4.31 \text{ mA}$

$$880 = \sqrt{880} \in$$

$$VPF = \sqrt{880} \in$$

EE - 973 MAM


c)

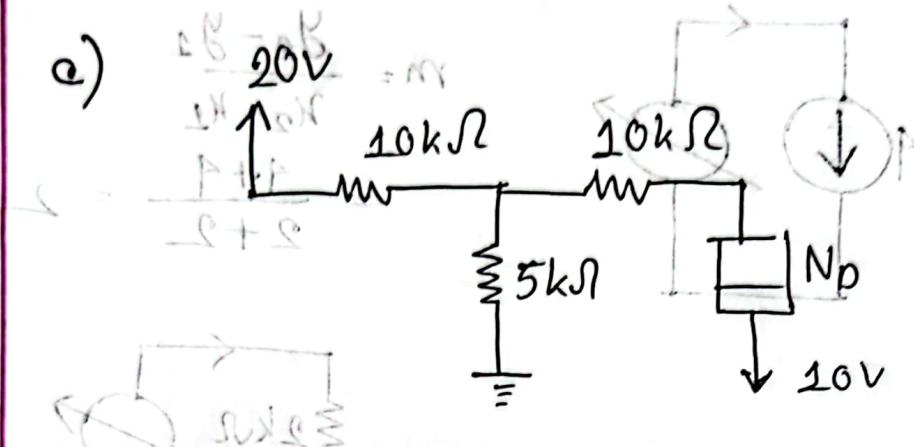

$$V = I \cdot R \quad (d)$$

$$8 \cdot 8 = 8$$

d)

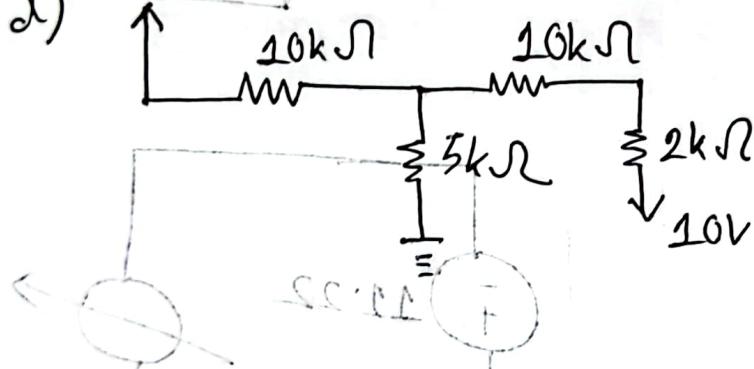


$$I = \frac{V}{R} + G \quad (e)$$

$$9 + \frac{9}{3.3} = 4 \quad (e)$$

$$4 \cdot 8 = 32$$

e)

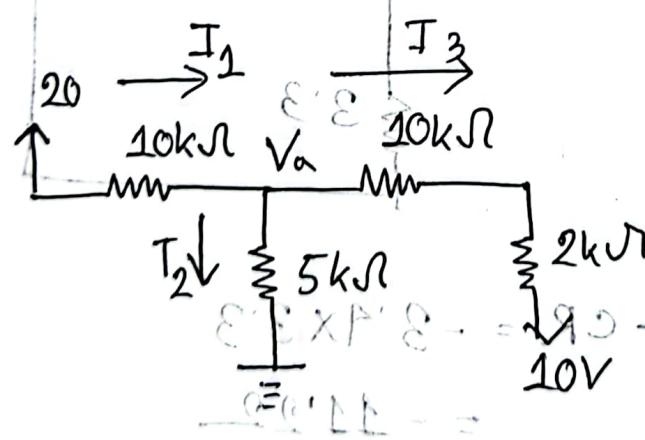

$$O = V$$

$$4 \cdot 8 = I$$

$$O = E$$

$$I_1 = 1.26 \text{ mA}$$

$$I_2 = 1.48 \text{ mA}$$

$$\frac{20 - V_a}{10} = \frac{V_a - 0}{5} + \frac{V_a - 10}{12}$$

$$I_3 = -0.22 \text{ mA}$$

$$\Rightarrow 2 - 0.1V_a = 0.2V_a + 0.083V_a - 0.83$$

$$\Rightarrow 0.383V_a = 2.83$$


$$\Rightarrow V_a = 7.9 \text{ V}$$

2) a) $ckt-1 \text{ w.r} \quad ckt-2 \text{ } y+z$


b) $f = (w.r) + (y+z)$

c) $f = (1.2). (3+4)$

$$= (F.R). (G+N)$$

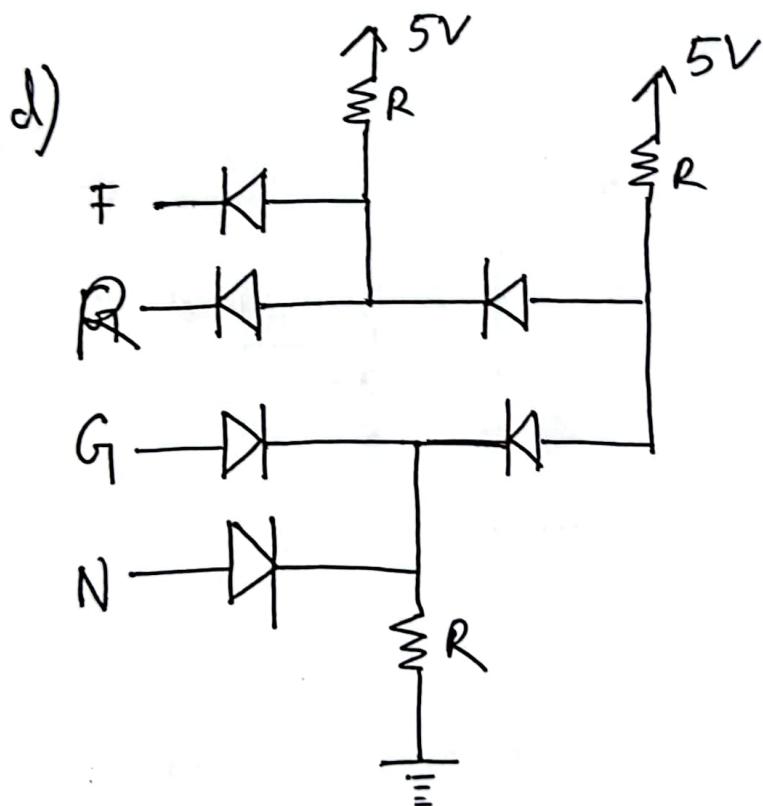

3) Assuming. D₁ ON, D₂ OFF

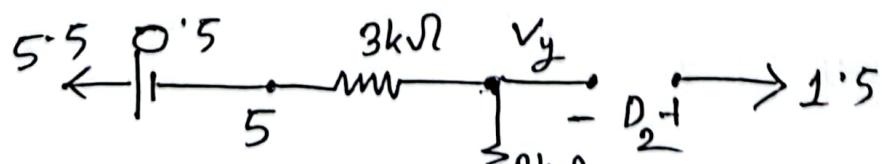

$$V_Y = \frac{2}{2+3} \times 5 = 2V$$


$$V_R = 5 \quad I_{D_1} = \frac{5-2}{3} = 1mA > 0$$

$$2 > 1.5$$

So, D₂ in reverse bias


Fall
Mid Sommer 2022

1) a)

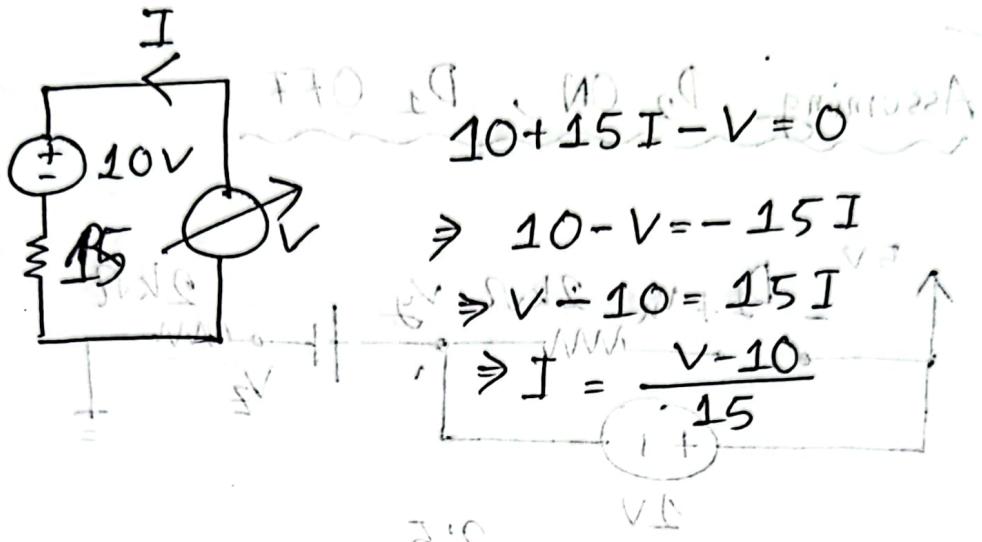


b)

$$I_D = 2 \times V_D + C$$

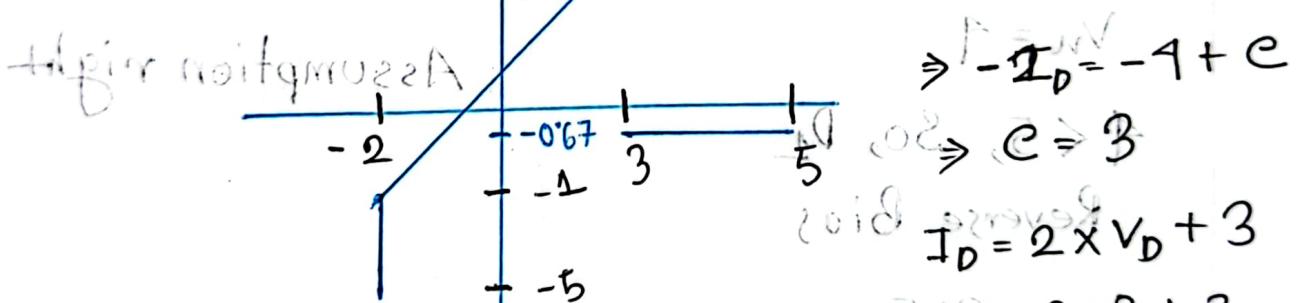


c)

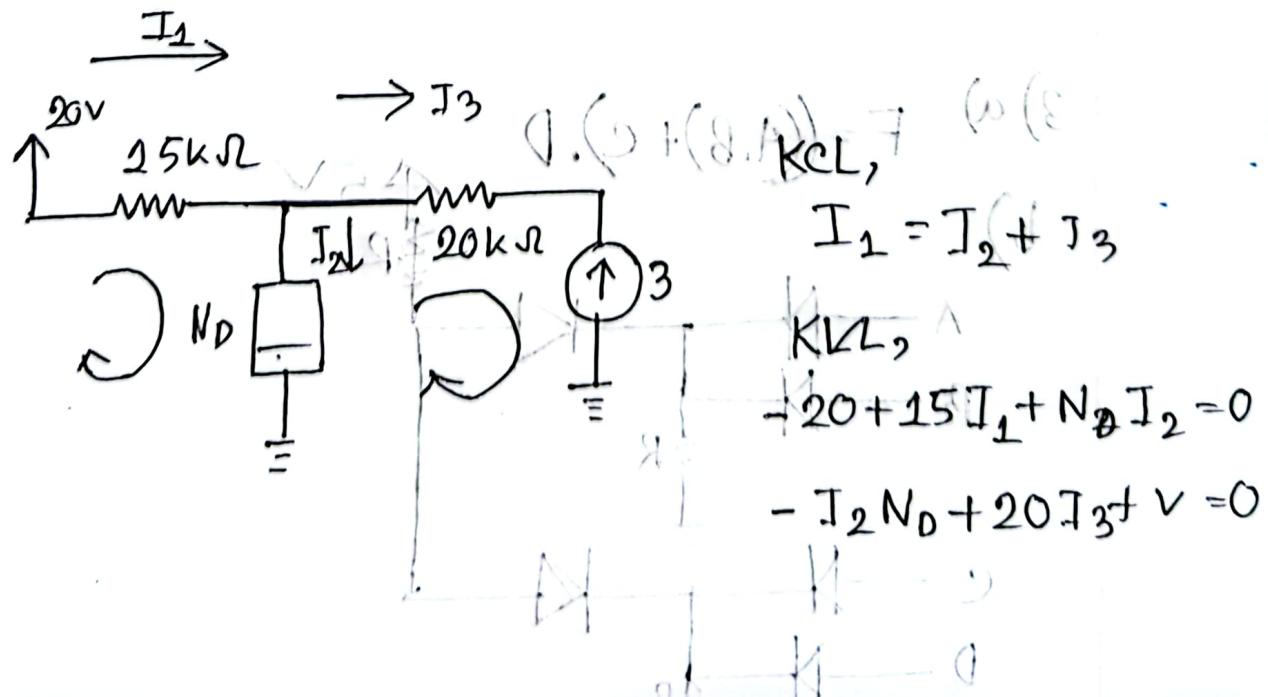

11.7
- 220Ω 75mV 2.6V

2)

Assuming D_2 ON, D_1 OFF

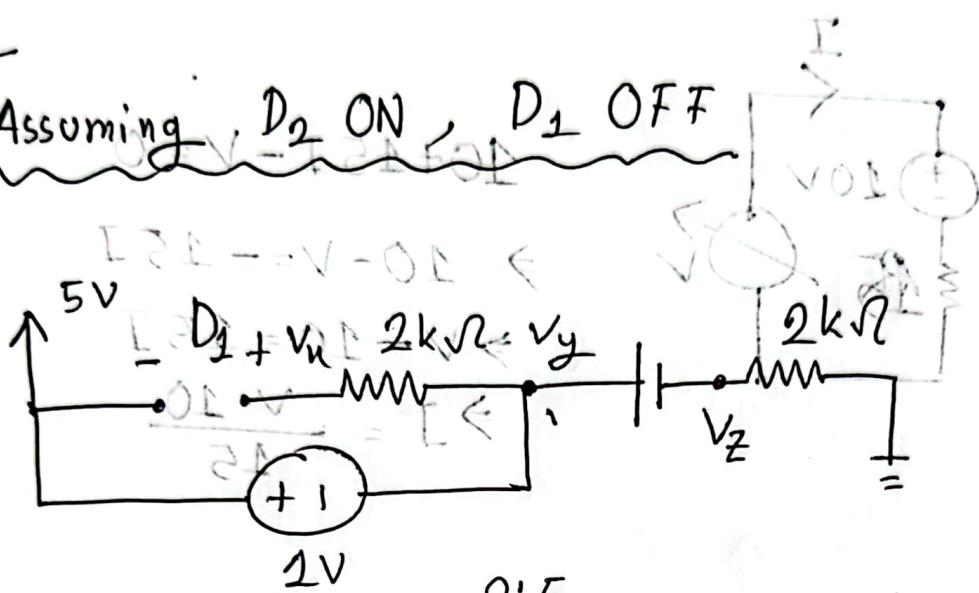

$$V_y = 1$$

$$I_{D_2} = \frac{5 - 0}{2} = 1.75 \text{ mA} > 0$$

$$V_u = 1$$

$4 < 5$, So, D_1

Reverse Bias


$$V_z = 3.5$$

Ans

Assumption right

$$3) a) F = ((A \cdot B) + C) \cdot D$$

$$b) F = A \cdot E$$

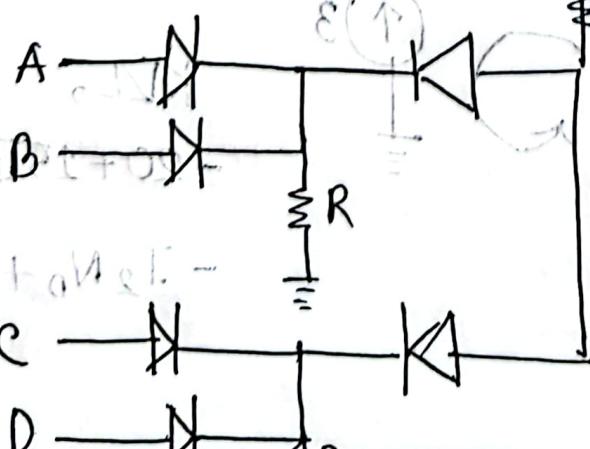

c)

