

|               |                          |            |
|---------------|--------------------------|------------|
| Assignment: 2 | Deadline: 25th july, 2pm | Marks: 100 |
| Q1-Q5: CO2    |                          |            |

### Q1. Diode logic gates.


[20]

a) Design a logic circuit using ideal diodes to implement the logic function  $f(A,B,C,D)$ . The function gives a logical high if all of the A,B,C inputs are simultaneously high or D is high.

b) Design an ideal diode based ckt. to get the largest voltage output from 3 voltages.


c) i) Deduce the logic function for the given circuit below.

 ii) what will be the output voltage if  $V_x=7V$ ,  $V_y=4V$ ,  $V_z=2V$  assuming both ideal model and CVD(0.7V) model.



### Q2-Q5 (Diode ckt solve using method of assumed states)

 Q2. Analyze the following circuit to find the values of  $I_{D1}$ ,  $I_{D2}$ ,  $v_x$ , and  $v_y$ . Here, use the Method of Assumed State using the CVD model of diode with  $V_{D0} = 0.7V$ . [20]



Q3) Solve the diode network ckt to find the  $V_a$ ,  $V_b$  and diode currents. [20]

(Solve using method of assumed states using the CVD model of diode with  $V_{D0} = 0.8V$ )



 


Figure - 1

 Q4) Solve the circuit **for the diode currents and voltages at all nodes**. Use the Method of Assumed State using the CVD model of diode with  $V_{D0} = 0.6V$  [20]



Q5)

 

**Analyze** the following circuit. **Calculate** the values of  $V_A$ ,  $V_0$ ,  $I_{D1}$ , and  $I_{D2}$ . You must validate your assumptions. Use the Constant-Voltage Drop model with a cut in voltage of  $0.6V$  [ $V_{D0} = 0.6V$ ]. [Hints: You may start with calculating the voltage values first]