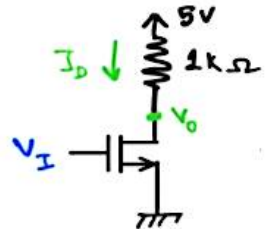


1. Construct the circuit with nmos switches and resistors to implement the logic functions [20]

a)  $A+B'C$    b)  $(AB+C+D)$    c)  $A'B+AB'$    d)  $(A'+B)'$

Solve the Q2-Q7 mosfet circuits using Assumed states method

2) What will be the change in the mosfet current if the  $V_i$  is changed from 2V to 5V. Assume  $k=2 \text{ mA/V}^2$ ,  $V_T=1 \text{ V}$  [15]




3) Find the gate voltage of the mosfet when the voltage at source node,  $V_s=1.5\text{V}$ . [10]




4) For figure-1,  $k=2 \text{ mA/V}^2$ ,  $V_T=1 \text{ V}$

i) Find the gate voltage so that the mosfet is in saturation mode.

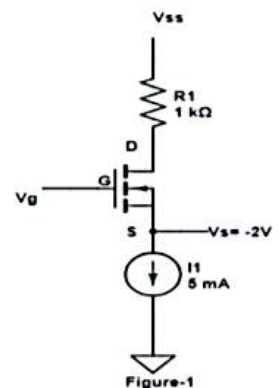ii) Then find the minimum supply voltage  $V_{ss}$  to operate the device in this condition. [Hints,  $V_{ov}=V_{DS}$ ] [10]



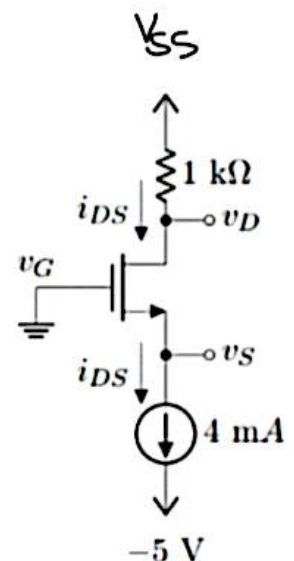
5) If  $V_{ss}=10\text{V}$  what is the value of drain voltage and source voltage? [10]



6) In the circuit above, the MOSFETs have the following parameters,  $k'_n = 2 \text{ mA/V}^2$ ,  $W/L = 2$ ,  $V_T = 1 \text{ V}$ .

a) What are the gate voltages of the mosfet?

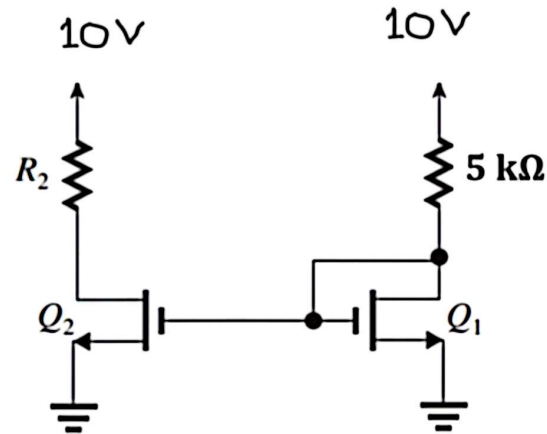b) for what value of  $R_2$  the  $Q_2$  mosfet will draw  $1 \text{ mA}$  current in the triode mode. [20]




7)

In the circuit shown in the figure below, the transistor is characterized by  $V_T = 1 \text{ V}$ ,  $k = 1 \text{ mA/V}^2$ . (Hint: Identify the modes of the two MOSFET, and equate the two currents.)

(a) [3 marks] Find the value of  $V_O$  indicated in the figure.

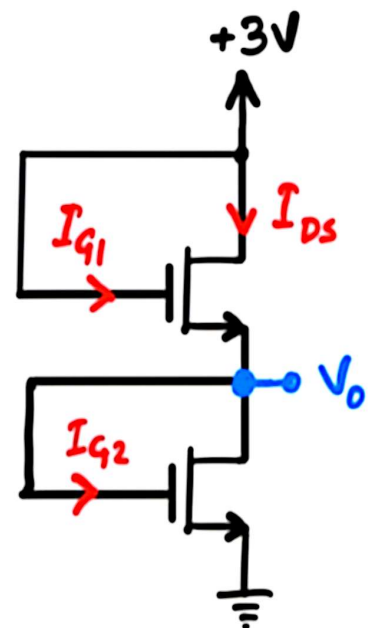(b) [3 marks] Find the values of  $I_{DS}$ ,  $I_{G1}$  and  $I_{G2}$ .



[15]